

University of Warwick

A Taste of Science and Engineering

Dr Leonardo Alves Dias



Topics

- Introduction to Arduino Platform: electrical engineering concepts.
- Introduction to programming concepts: using block-based programming.
- Introduction to development platforms: Tinkercad.
- Prototyping with Arduino: practising programming and electronics.
- Introduction to sensors and actuators.



Learning outcomes

- Understand and explain concepts of microcontrollers.
- Understand basic concepts of electronic devices.
- Understand basic concepts of visual programming using block-based programming.
- Simulate electronic prototypes.



1. Introduction to Arduino

Introduction



Created in mid-2005.



Developed in Italy to create projects/prototypes in a simple and faster way.



Arduino is a programmable electronics prototyping platform based on microcontrollers (Atmel) used in the control of logical processes.




Open-Source Platform: free hardware and software.



<https://www.arduino.cc/>

Introduction to Microcontrollers

- A microcontroller is a programmable integrated circuit that executes orders stored in its memory. It can also be defined as an integrated circuit with “programmable intelligence” used to control logic processes.
- They are generally used in the automation and control of products and peripherals, such as automotive engine control systems, remote controls, office and home machines, toys, supervisory systems, etc.

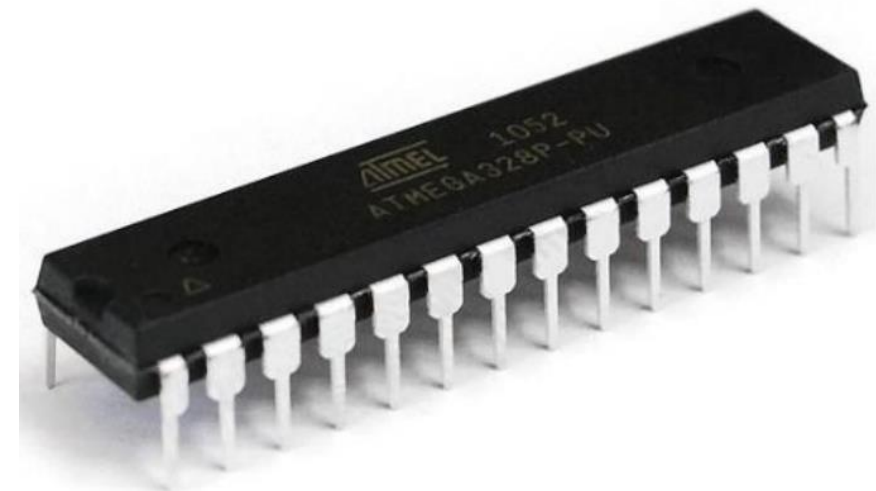

Applications of Microcontrollers

Telecommunication, Robotics, Home appliances, Healthcare, and Industrial, among others.



Internet of Things


- The Internet of Things (IoT) is a concept that refers to the interconnection of everyday objects and devices to the Internet, enabling them to collect, exchange, and act on data without the need for direct human intervention.
- It extends the capabilities of traditional devices by granting them the ability to communicate, analyse, and respond to data in real-time.
- IoT has the potential to transform various industries, enhance efficiency, and improve the overall quality of life.
- Application examples: smart home devices, smart cities, healthcare, industrial, agriculture, connected vehicles, etc.

Internet of Things – Arduino Applications

Smart Home Devices:

IoT enables various devices to be interconnected to enhance convenience and energy efficiency.

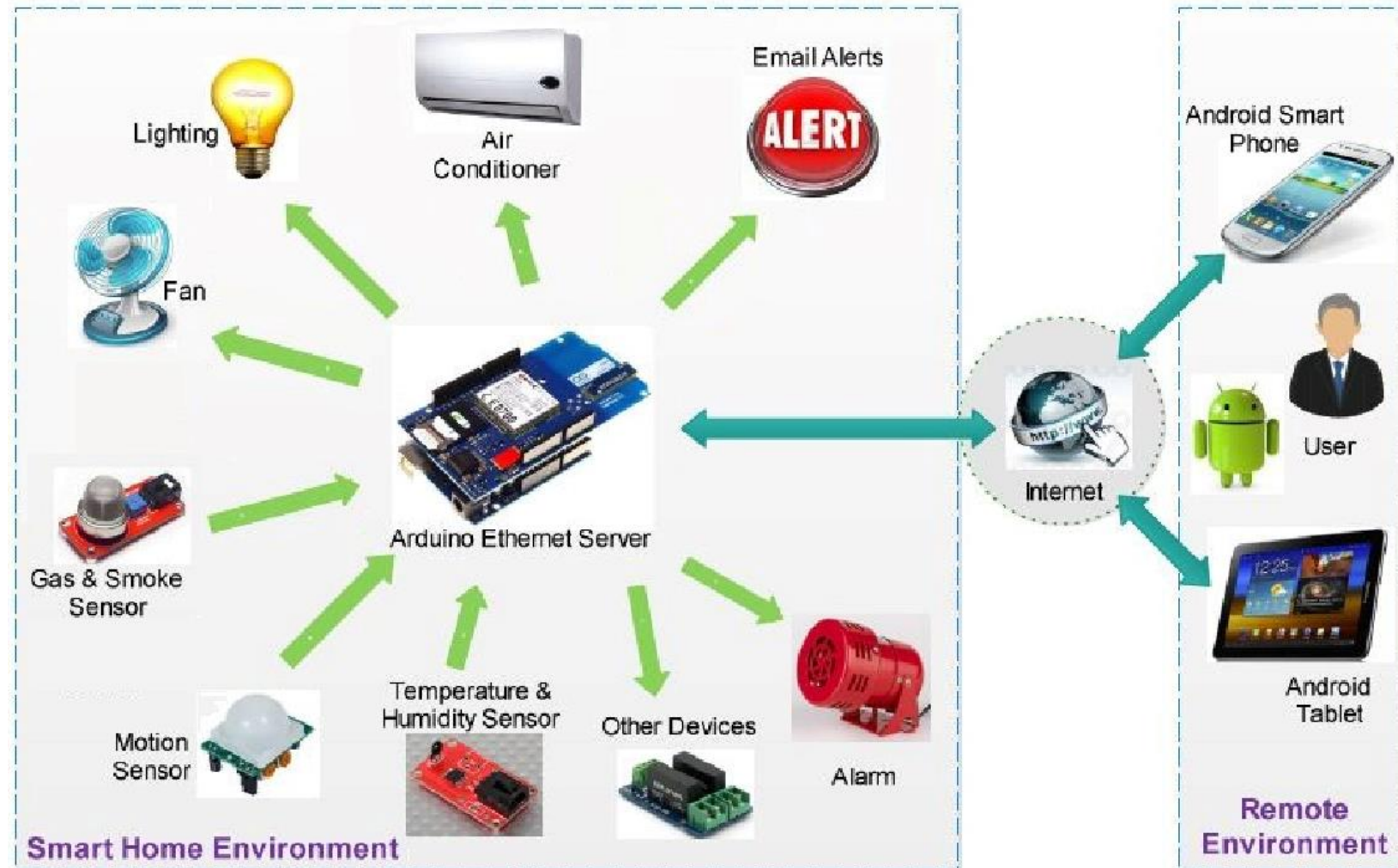Examples include smart thermostats, smart lighting systems, voice-controlled virtual assistants (such as Amazon Echo or Google Home), and connected security cameras, amongst others.



Introduction to Arduino Platform

Arduino Family:

Arduino Leonardo




Arduino Mega2560 R3



Arduino Industrial 101



Arduino Ethernet

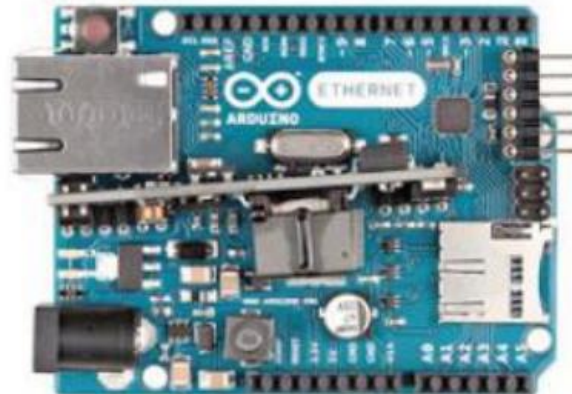


Arduino M0




Introduction to Arduino Platform

Arduino Family:


Arduino Yún

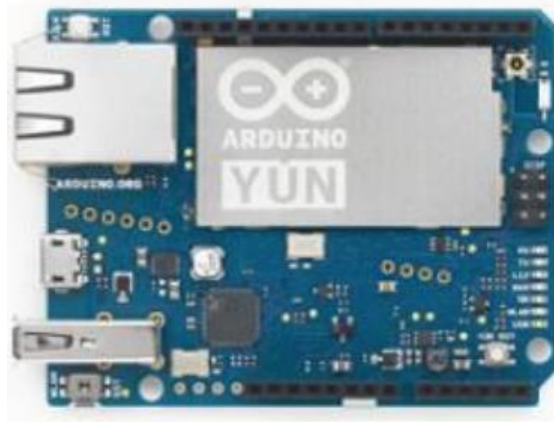

Arduino Leonardo Ethernet

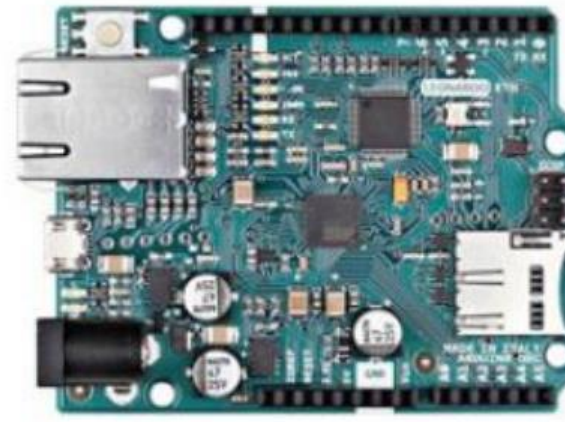

Arduino LilyPad

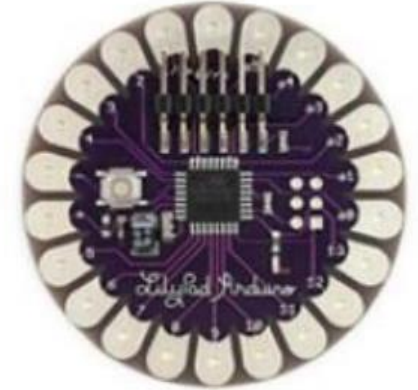


Arduino ISP



Arduino Yún mini



Arduino Micro

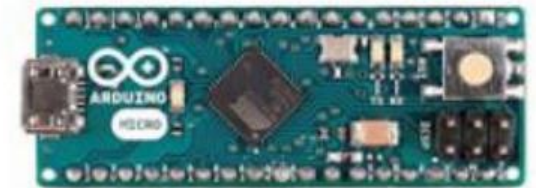


Introduction to Arduino Platform

Arduino Shields: A board that allows you to expand the functionality of the Arduino.

Arduino Ethernet Shield R3



Motor Shield R3

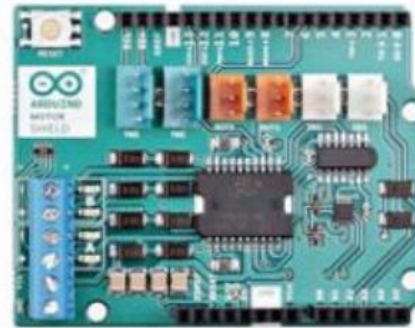


Arduino WiFi Shield



Shield Arduino 4 relês




Arduino ProtoShield R3

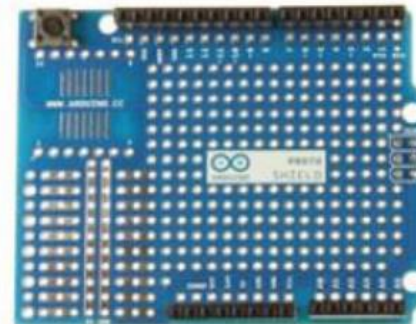

Arduino USB Host Shield




Arduino Board

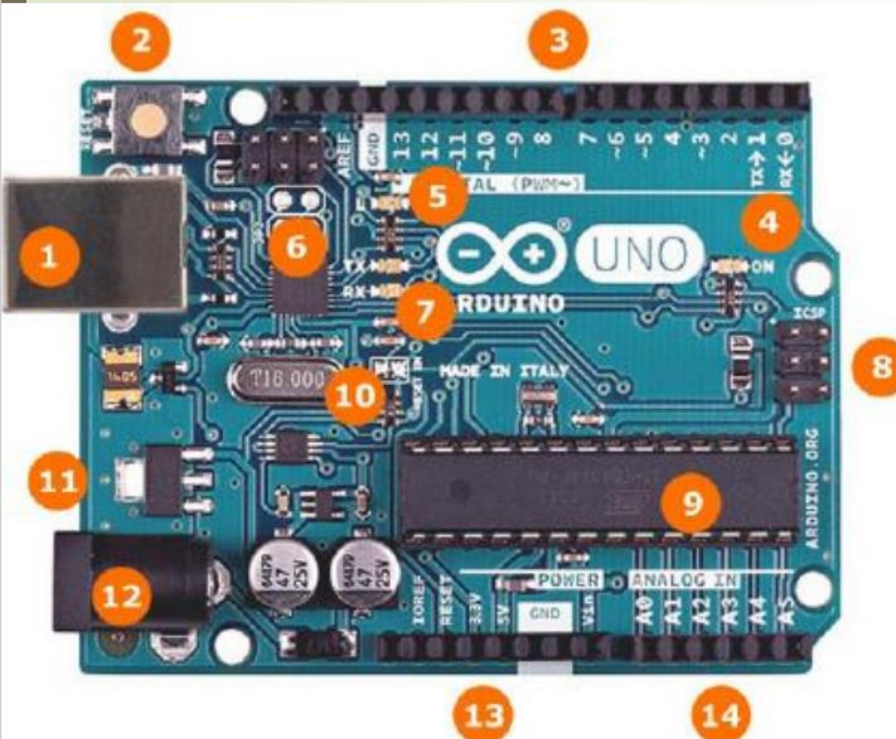

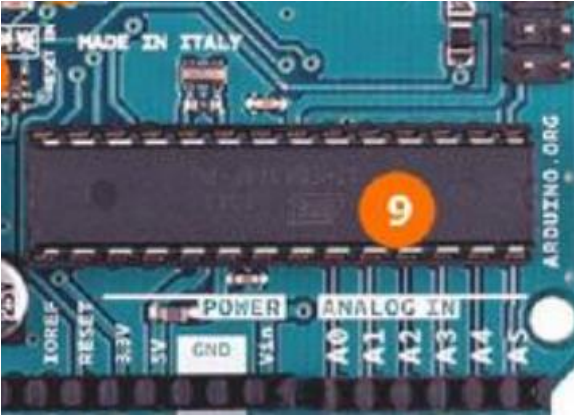1. Power (USB Connector).
2. Reset Button.
3. Digital input/output pins and PWM
4. Power LED.
5. LED connected to pin 13 (used for board testing).
6. PC Communication Microcontroller (ATMEGA).
7. Serial communication LEDs (TX/RX).
8. Serial communication (ICSP).
9. ATMEGA Microcontroller.
10. Crystal Oscillator (16MHz).
11. Voltage Regulator.
12. Power (Barrel Jack/Wall Power Supply).
13. Arduino source and ground pins.
14. Analogue inputs.

ATMEGA Microcontroller

- Microcontroller present: ATMEGA 328P.
- Operating voltage: 5V.
- I/O (Input/Output) pins: 14 (6 can be used as PWM(~)).
- Continuous current: 20mA (5V), 50mA (3.3V).
- Flash memory: 32kB.
- SRAM memory: 2kB.
- EEPROM memory: 1kB.
- Clock: 16MHz.



Summary

We introduced the concepts of a Microcontroller. ✓

We introduced the family of Arduino Boards. ✓

We introduced the ATMEGA microcontroller present on the Arduino UNO. ✓

2. Arduino: Development platforms

Arduino Simulators

- Arduino IDE: <https://www.arduino.cc/en/software>
- Proteus: <https://www.labcenter.com/>
- SimulIDE: <https://sourceforge.net/projects/simulide/>
- TinkerCAD: <https://www.tinkercad.com/circuits>

Tinkercad: Creating an account

1. Click on Sign Up to create your account.
2. Click on Create a personal account (On your Own) and Sign Up with an Email.
3. Add your Country and Birthday.
4. Add your email and create a password.
5. Click “Done!”


Observation: You will need to check your email and verify your account

Joining a Tinkercad Class

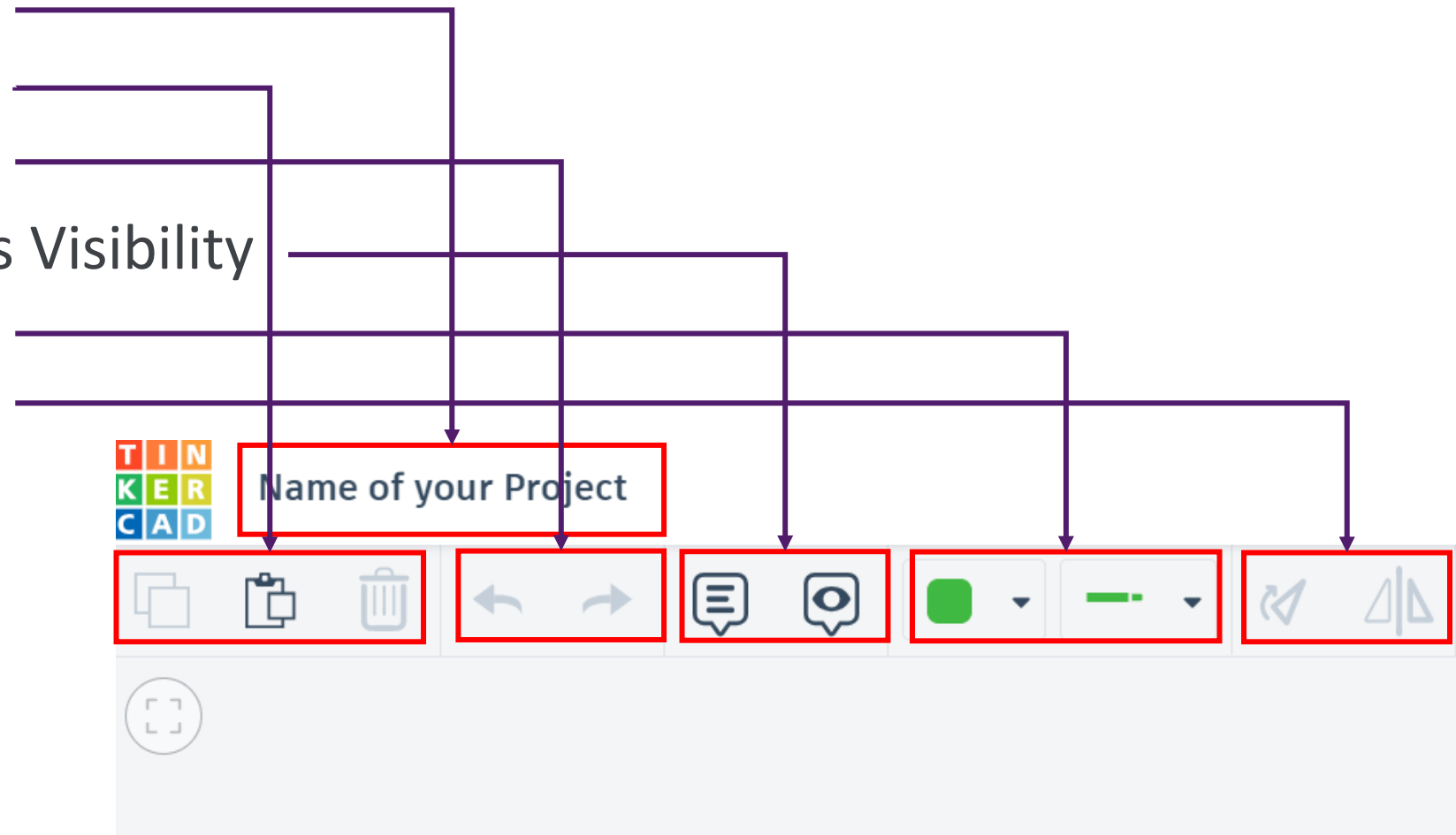1. Click on “Classes”
 2. Click on “Join a class”
 3. Use the code TWQ-I2X-2LI-PLU and click Go to My Class. Alternatively, click on the link: <https://www.tinkercad.com/joinclass/TWQI2X2LIPLU>
 4. Click on “That’s me.”
- You now have the Warwick Summer School class. Inside this class, you will find the activities for this course.


Tinkercad User Interface

- Name of your project.
- Copy, Paste, Delete
- Undo, Redo.
- Add Notes, Toggle Notes Visibility
- Wire colour and type
- Rotate and Mirror.



Tinkercad User Interface

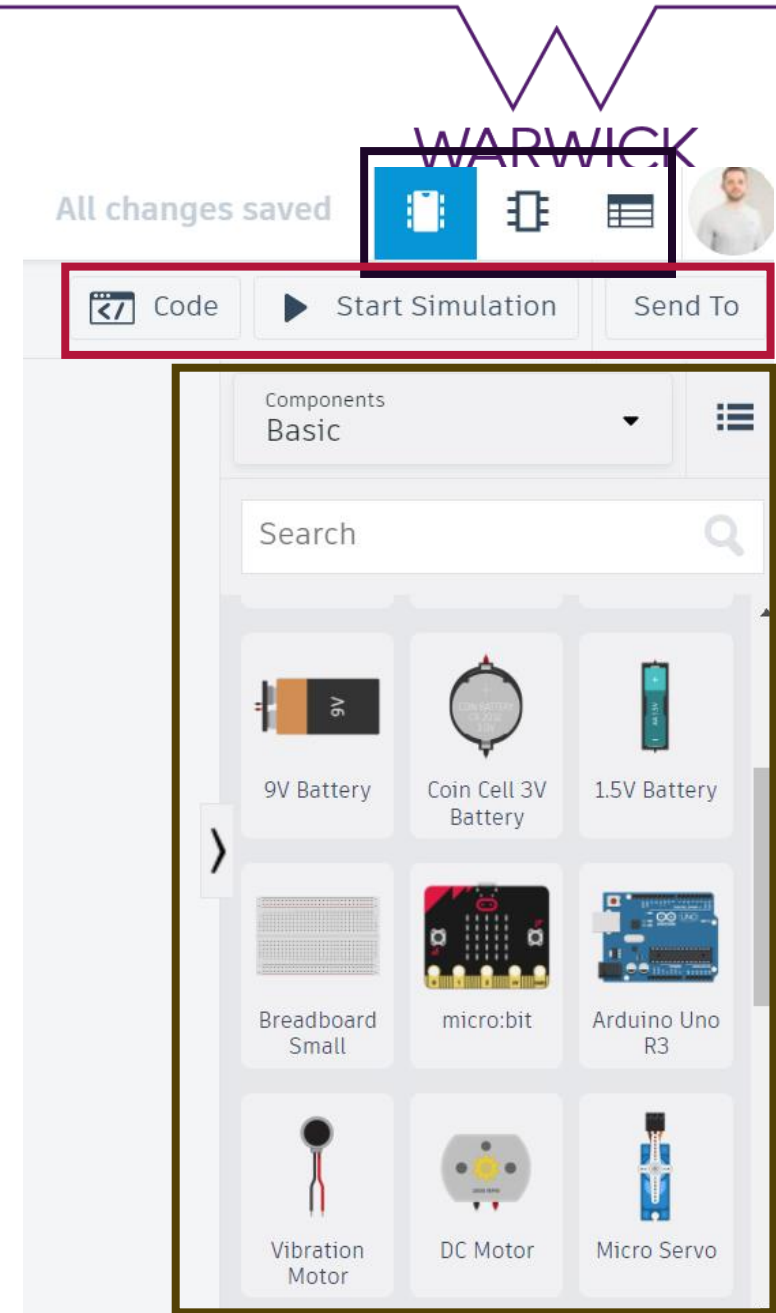- Circuit View
- Schematic View
- Component list.
- Code
- Start Simulation
- Send to
- Components.
- Search Bar
- Component Menu.




Summary

We introduced different Arduino Platforms for learning and practising. ✓

We learned how to create and account on TinkerCAD. ✓



We introduced the TinkerCAD circuit simulation user interface. ✓

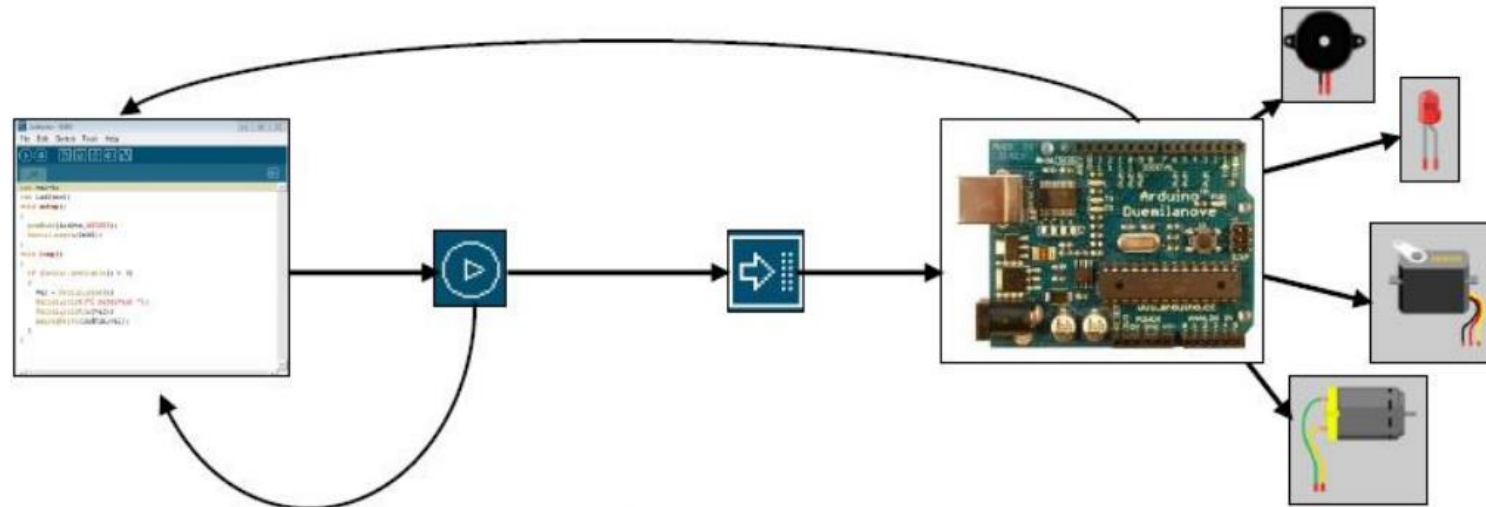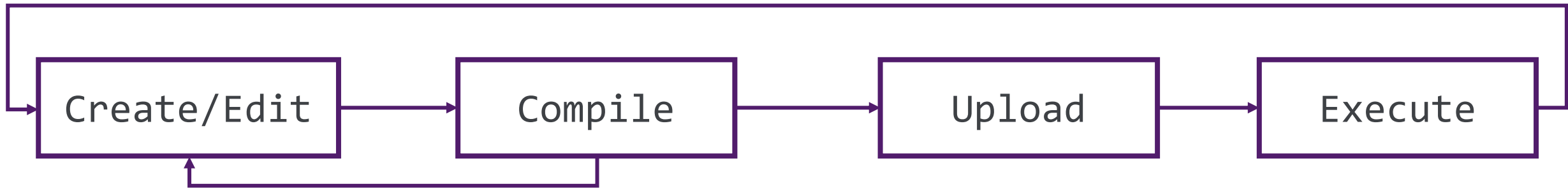3. Arduino: Prototyping



Prototyping

A prototype is developed based on the following step-by-step:



Input/Outputs

- The inputs, or inputs, are usually electronic or mechanical sensors that convert signals (in the form of temperature, pressure, humidity, contact, light, movement, pH, etc.) from the physical world and convert them into current or voltage signals. Examples of inputs are photocells, potentiometers, gas, temperature, movement sensors, etc.
- Outputs are actuators or other devices that convert current or voltage signals into physically useful signals such as movement, light, sound, force or rotation. Examples of outputs are motors, LEDs or lighting systems, a buzzer that generates different tones, etc.

Input:

Receive signals from the physical world and convert them into current or voltage



Processing:
Interpret and manipulate signals

Output:

Convert current or voltage into physically useful signals

Types of Signals

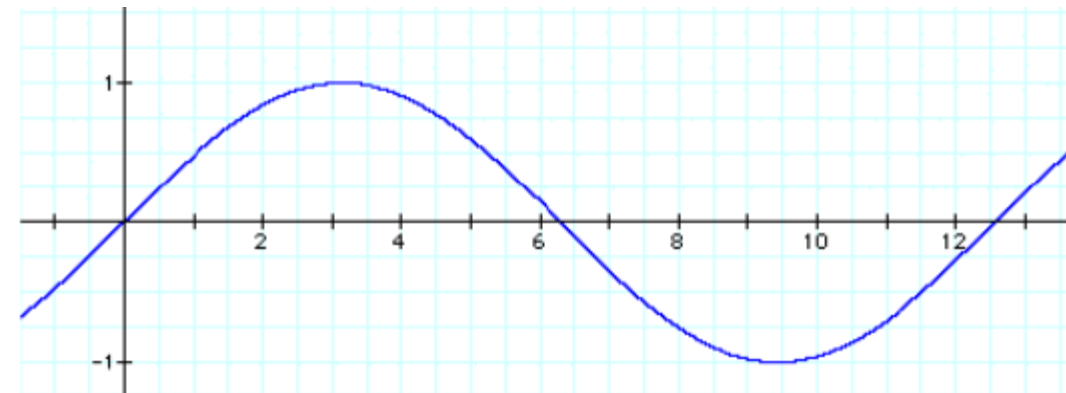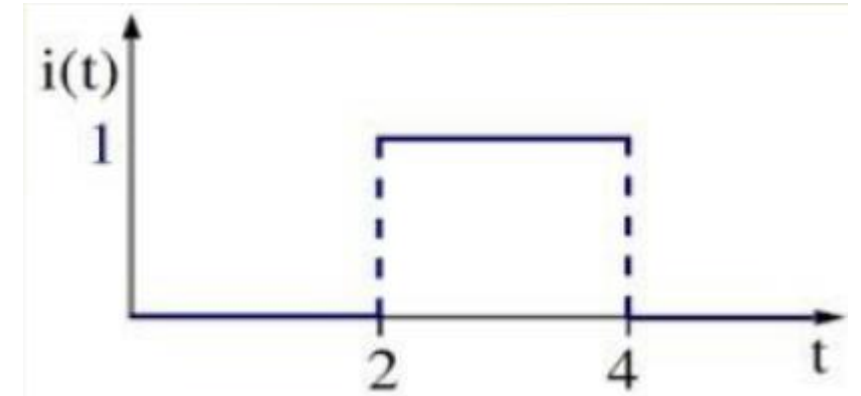- Digital:
Works according to Boolean principles: bit 0 represents 0V (volts), and bit 1 represents 5V (volts).
- Analogue:
Time-varying signals (constantly take on different values)




Hello World

- This example shows the simplest experiment you can do with an Arduino to verify a physical output: blinking an LED. In this example, you will learn how to drive a load (built-in LED) connected to an Arduino pin.


i What will I learn?

- Activate a digital output.
- Blink the on-board LED.
- The syntax of an Arduino Code.
- Use timers on an output pin.

i Components


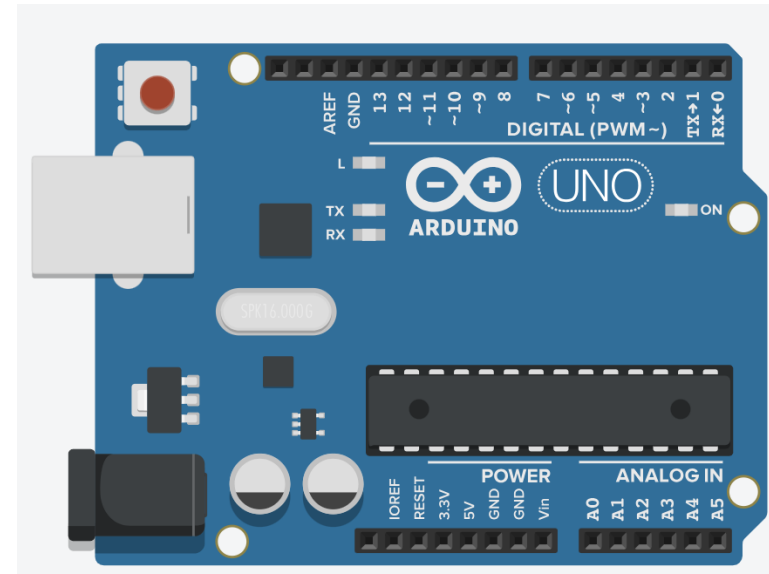


Hello World

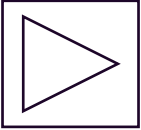


The Code

- Control Structures (Yellow):
 - on start: code structure that can be used to execute blocks of code only once and when the board is powered. Use it for code that you only want to execute once when the board is turned on.
 - forever: code structure that can be used to execute code blocks repeatedly in an infinite loop while the board is powered. Use it for code that you want to be constantly executed while the board is turned on.

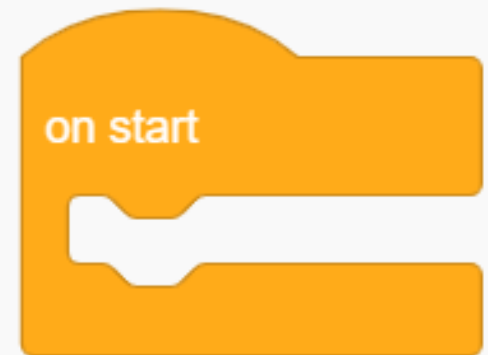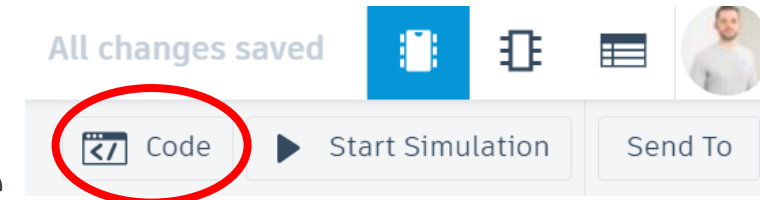


Hello World

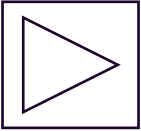

The Code

- Control Commands (Yellow):
 - wait: this code block activates a timer. The microcontroller waits for the defined time to be over before executing the next code block. For this example, the timer was set to 1 second.
- Output Commands (Blue):
 - set built-in LED: define the logical value on that pin. The pin will work as an output, controlling anything connected to it. Built-in LED is the name given to pin 13.

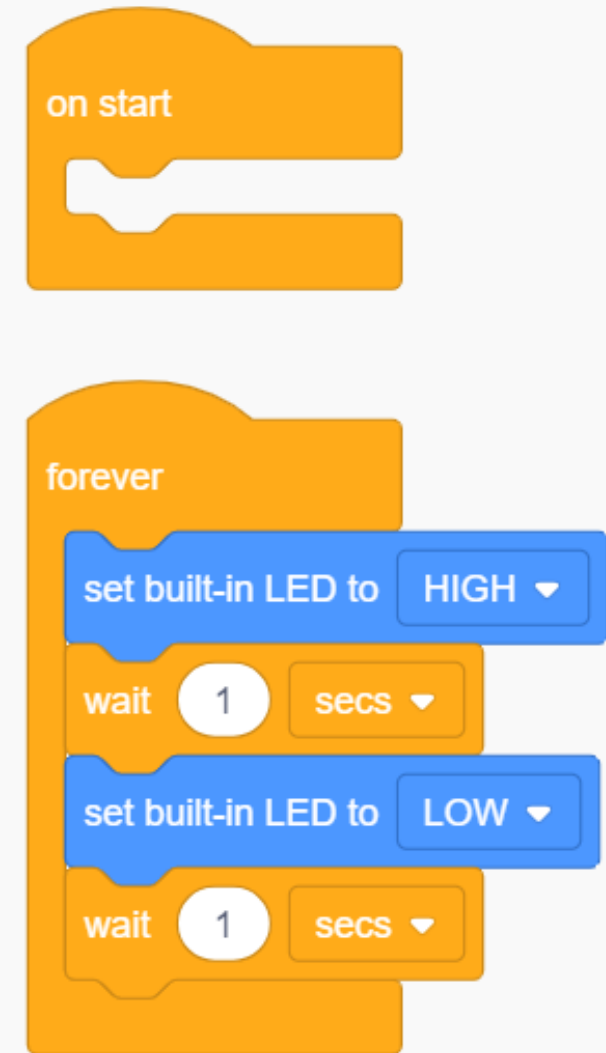



Hello World

The Code

The “set” command is used to write on the pin, i.e., to send a logical value to that pin.

```
forever
  set built-in LED to HIGH
  wait 1 secs
  set built-in LED to LOW
  wait 1 secs
```

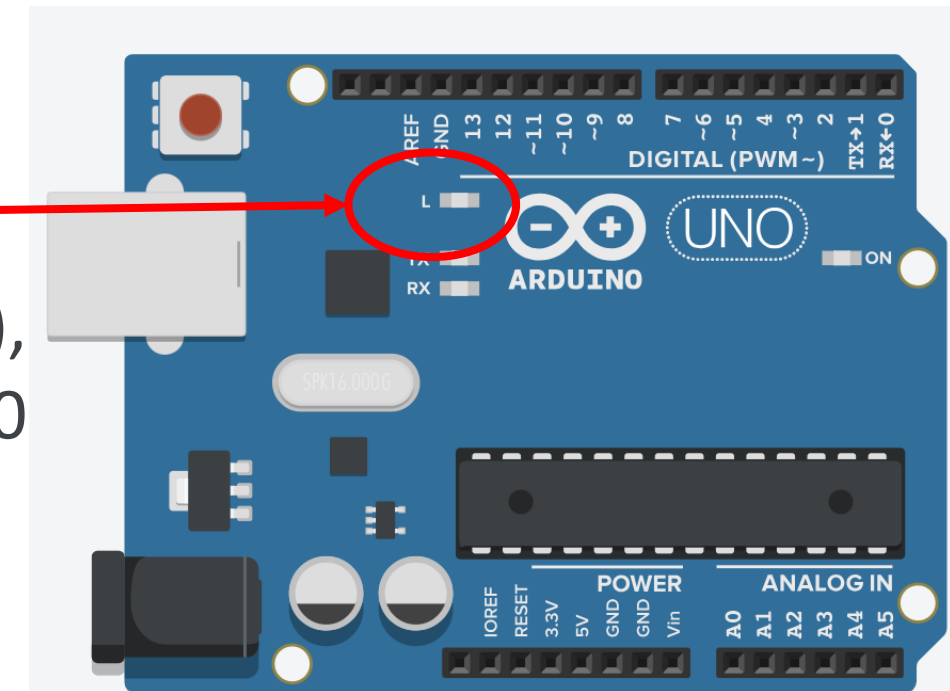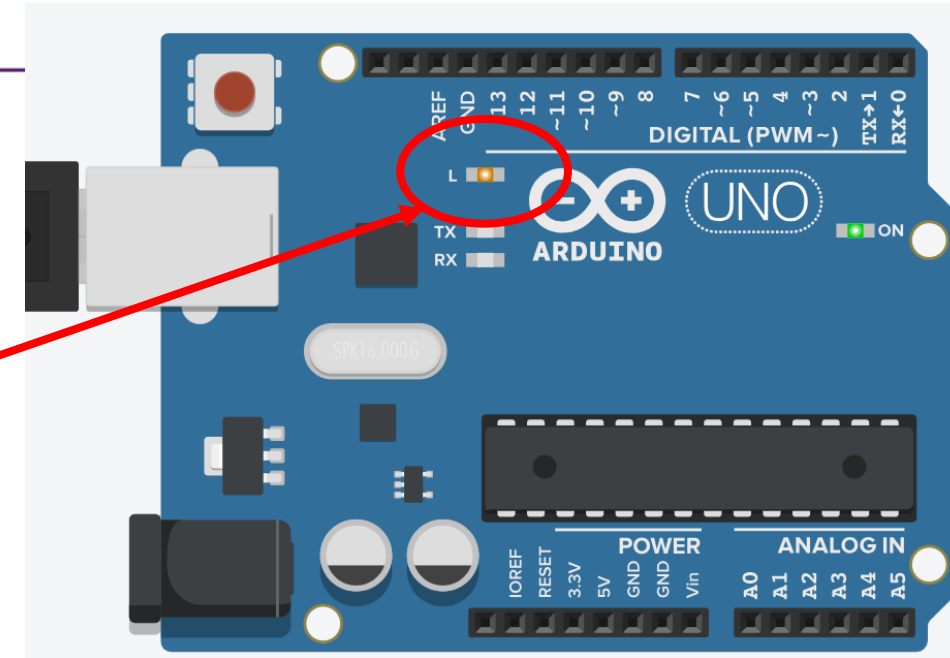HIGH is equivalent to bit 1 (5V), while **LOW** is equivalent to bit 0 (0V).





Hello World – External LED

- This example is similar to the previous one: blinking an LED. In this example, you will learn how to drive a load (an external LED) connected to an Arduino pin.

i What will I learn?

- Activate a digital output.
- Blink an LED external to the board.
- The syntax of an Arduino Code.
- Use timers on an output pin.

i Components

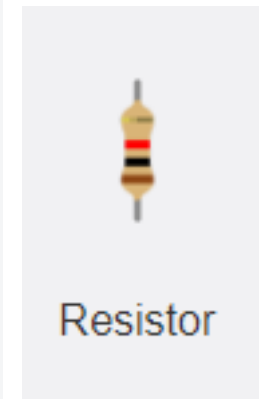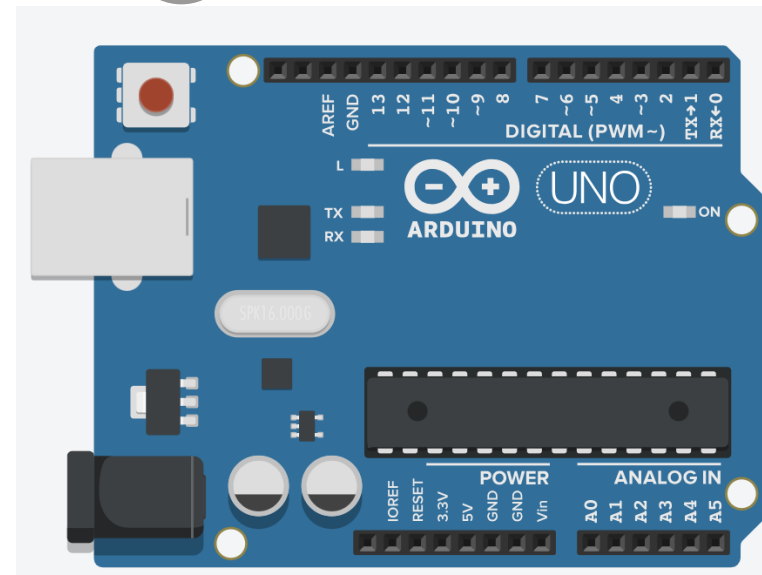


Resistor




LED

Hello World – External LED

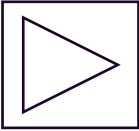

The Code



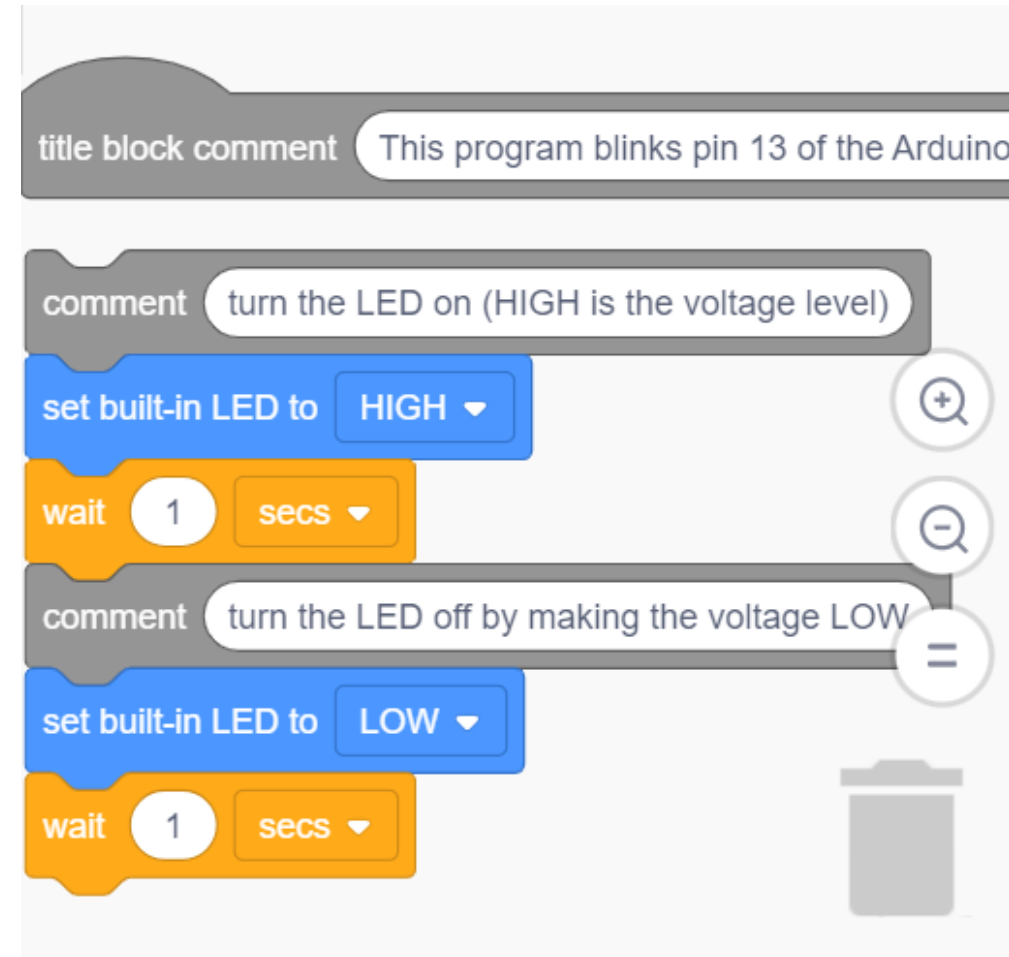
- Notation (Grey):
 - The notation blocks are used to add comments to your code. Comments are helpful for others to understand your code, and they do not execute any action.




Hello World – External LED

The Code

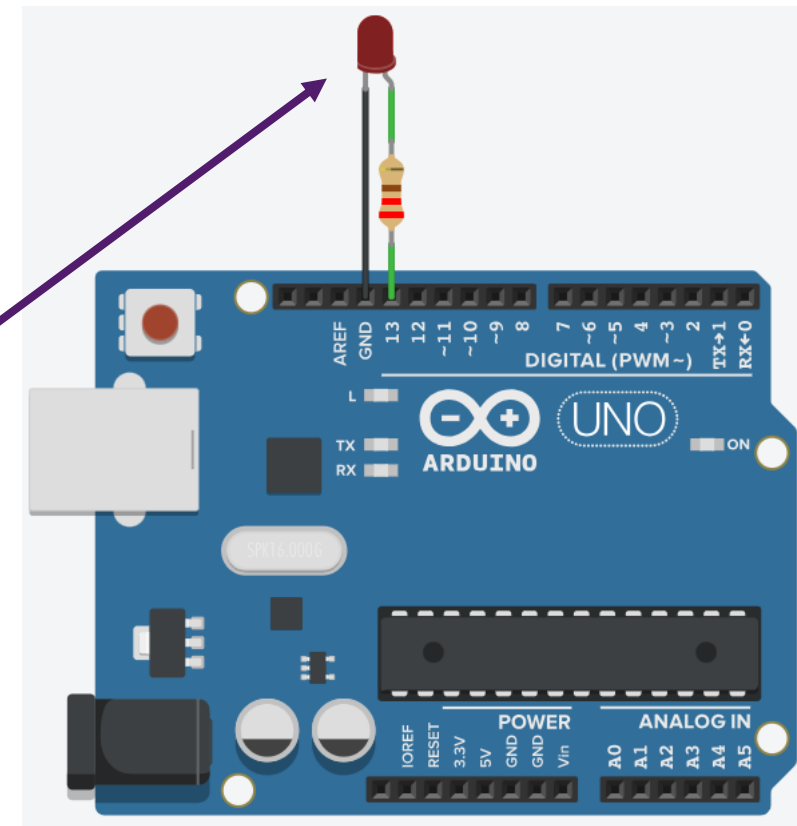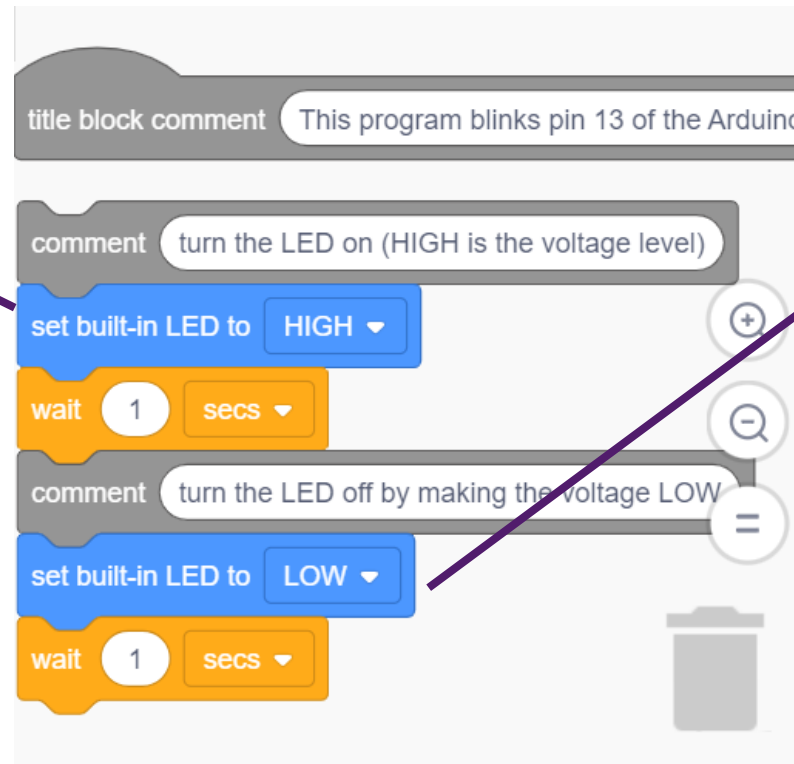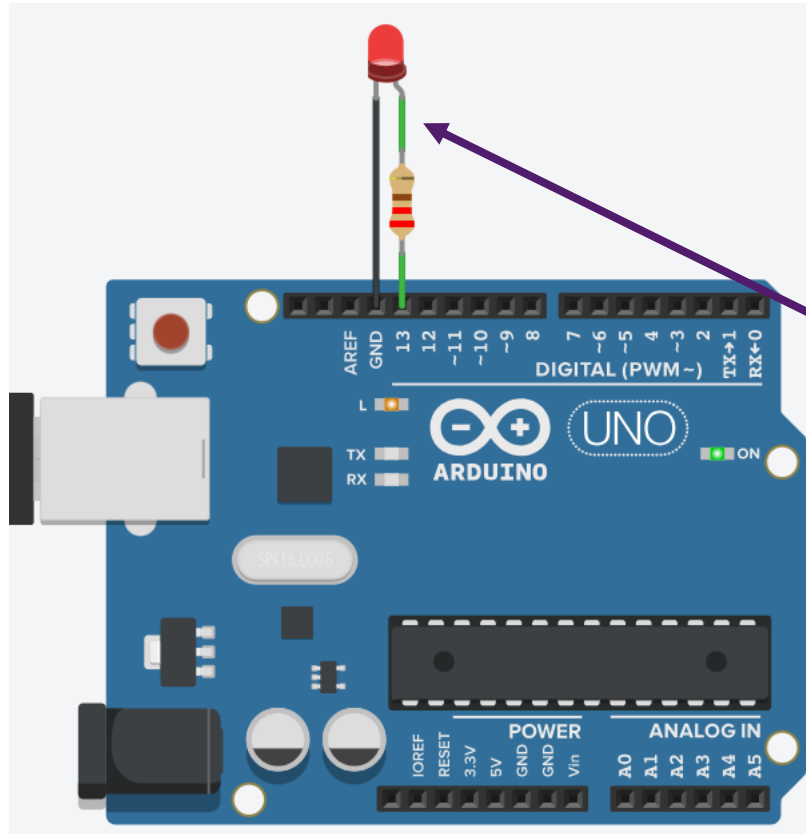
- Note that the program executes repeatedly despite not using the forever block.



Hello World – External LED

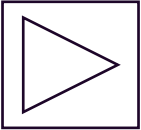

The Circuit



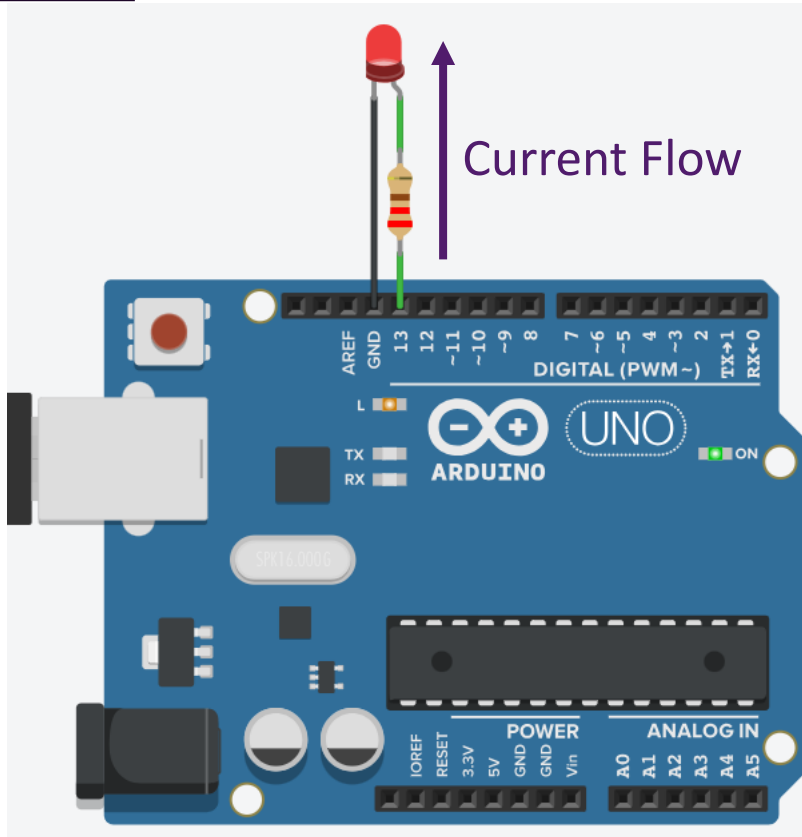


- When an Arduino pin is used as an output, it supplies the load connected to it a total of 5V and 20mA.
- This is enough to damage an LED. Therefore, a resistor is necessary to limit the amount of current that goes to the LED.
- Hence, a resistor was connected between the output pin 13, the LED and the ground (GND), reducing the current (I) from its maximum value ($I < 20$).


LED (Light-Emitting Diode)

The Circuit

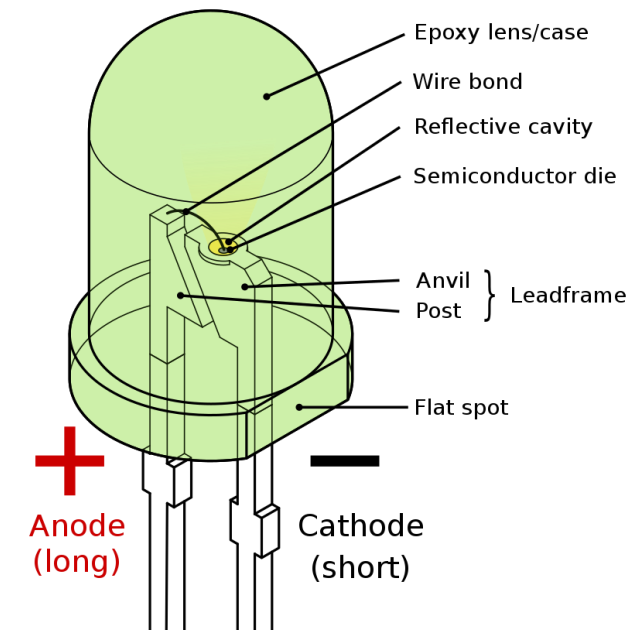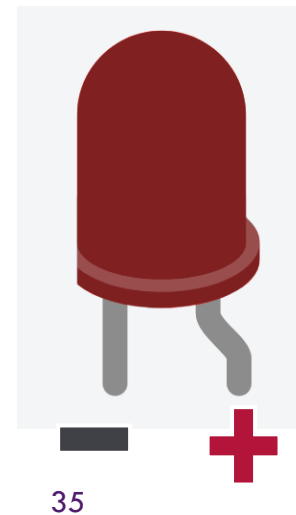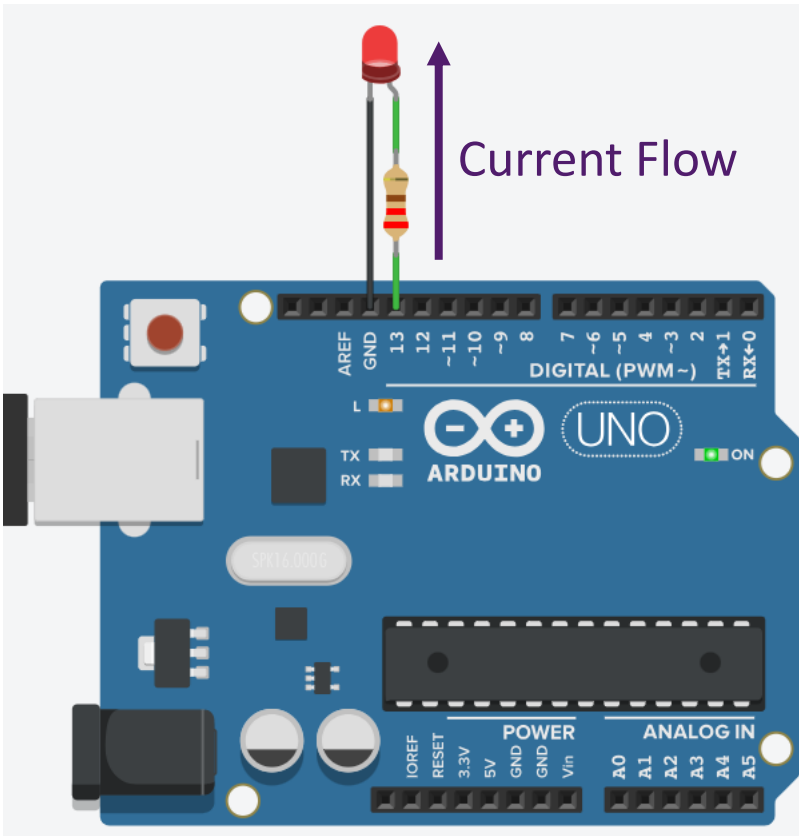
- A LED (light-emitting diode) is a semiconductor device that emits light when current flows through it.
- The LED terminals are called: anode (+) and cathode (-).




LED (Light-Emitting Diode)

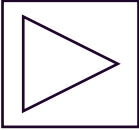


The Circuit

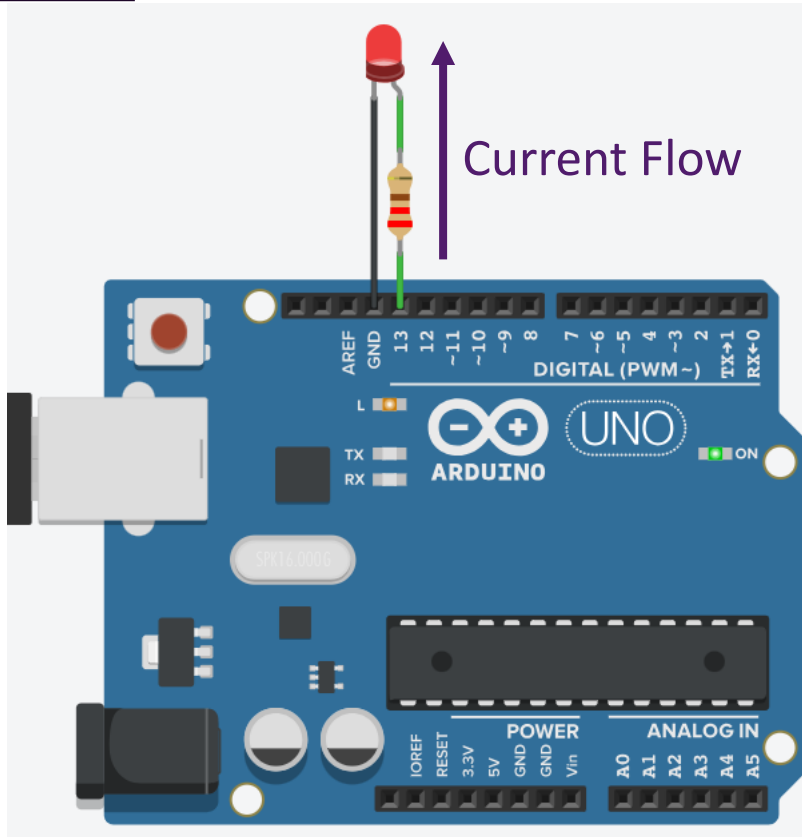

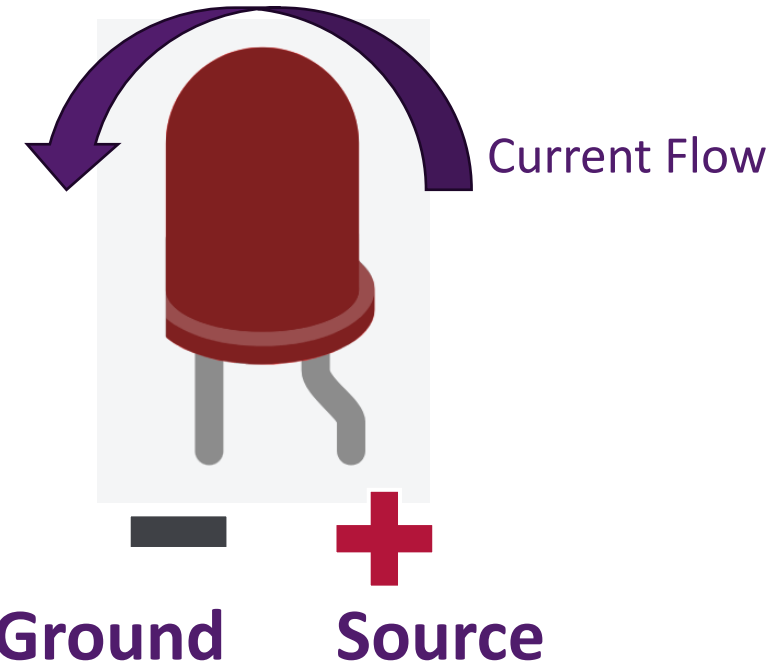
- The LED has a polarity, that is, a connection order. Changing this order will make it not work properly.
- Hence, for it to work, the current must flow from the anode (+) to the cathode (-).



Resistor

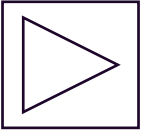

The Circuit

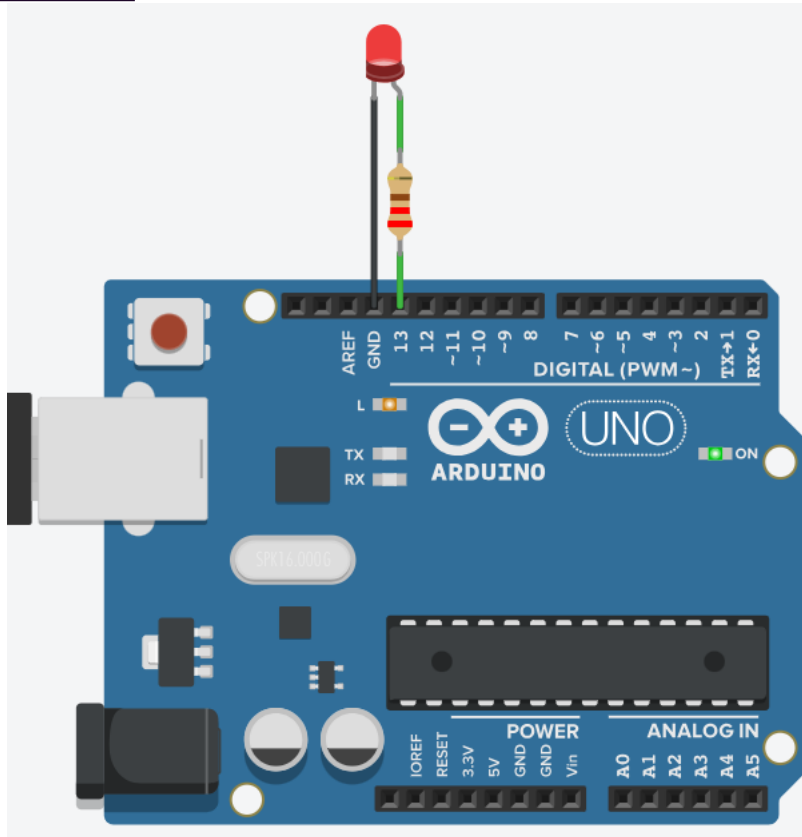



- A resistor is a passive two-terminal electrical component that implements electrical resistance.
- In electronic circuits, resistors are used to reduce current flow and divide voltages, among other uses.
- Ohm's law states that the resistance can be defined based on the voltage (V) and current (I), as follows:

$$R = \frac{V}{I} \Omega$$

Resistor

- The resistance value of a resistor can be defined based on its colour code:
- To change its value on Tinkercad, click on the component and modify its value in the pop-up box.

The Circuit

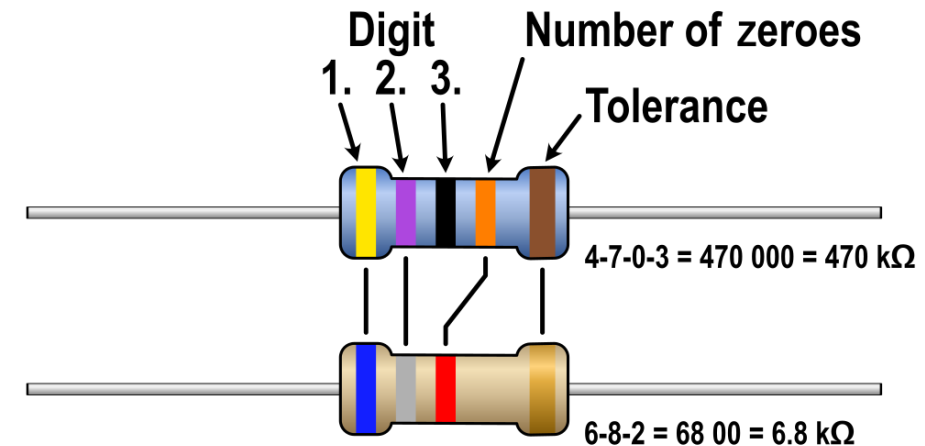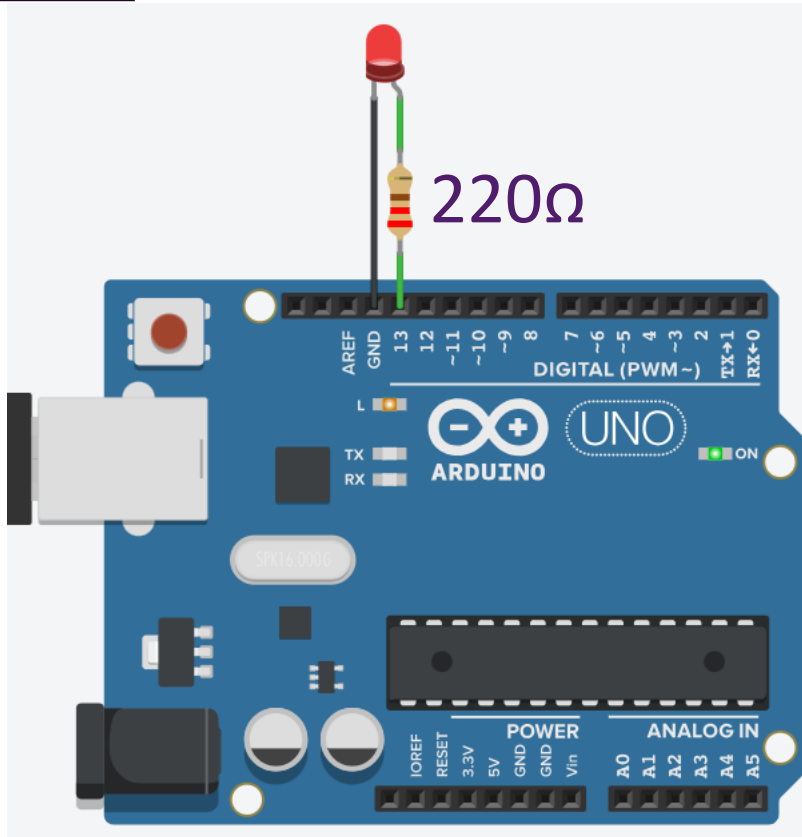


Digit	0	1	2	3	4	5	6	7	8	9



Tolerance	Silver ±10 %	Gold ±5 %	±1 %	±0.5 %	±0.1 %

External LED in different Digital pins

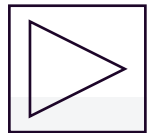The LED can be connected to other digital pins. For example, let's replace pin 13 in the previous example to pin 10.




The Circuit

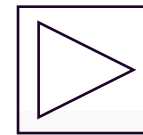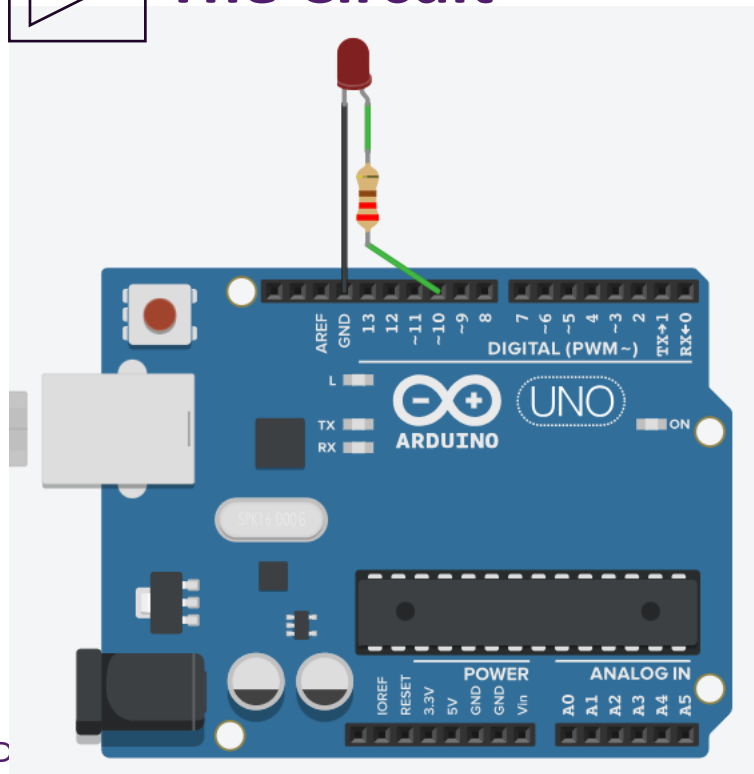

The Code

```
title block comment This program blinks pin 10 of the Arduino

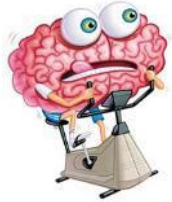comment turn the LED on (HIGH is the voltage level)
set pin 10 to HIGH
wait 1 secs
comment turn the LED off by making the voltage LOW
set pin 10 to LOW
wait 1 secs
```



Practice Questions

1. Modify the Hello World with an External LED example, as follows:
 - a) Make the LED stay 3 seconds ON and 3 seconds OFF.
 - b) Make the LED stay 200 milliseconds ON and 500 milliseconds OFF.
2. Again, from Hello World with an External LED example, make the necessary changes in the code and circuit so that the LED is placed on Pin 5, and stays 2 seconds ON and 1 second OFF.


Multiple LEDs

- In this example, you will learn how to drive three loads (LEDs) connected to an Arduino pin.


i What will I learn?

- Activate multiple outputs simultaneously.
- Use a breadboard.
- Use Arduino source and ground pins

i Components

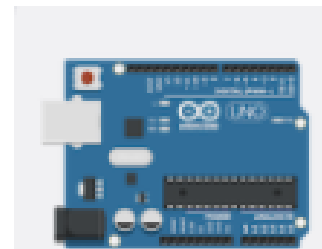

Arduino Uno
R3

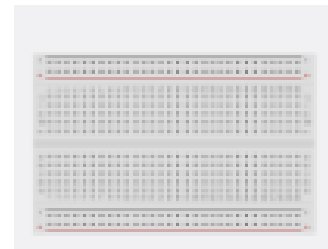

Breadboard
Small




Resistor




LED

Multiple LEDs

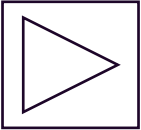


The Circuit

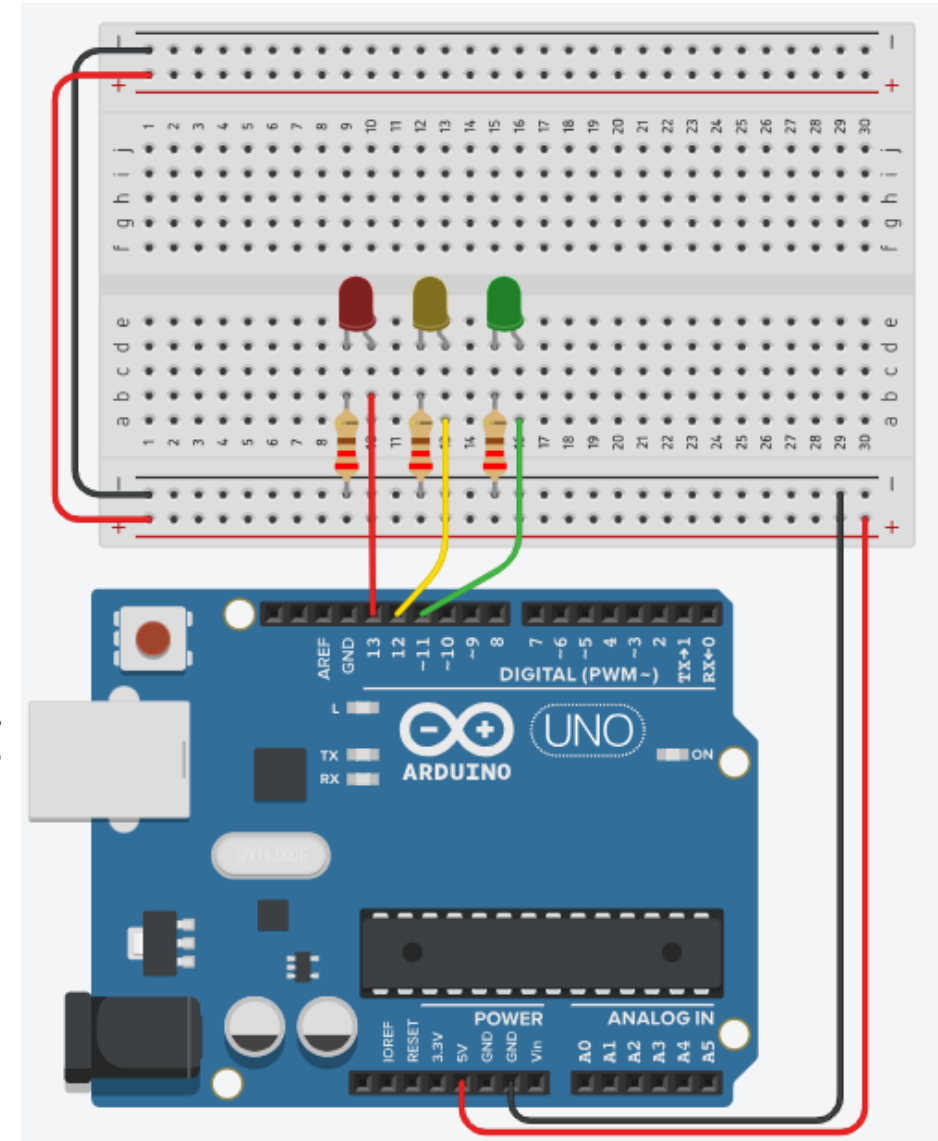- You will need:
 - 1 Arduino Uno board.
 - 3 LEDs (Click on it the change its colour).
 - 2 Resistors (220 Ω).
 - 1 Breadboard.
-
- Connect all components like in the following image:






Breadboard

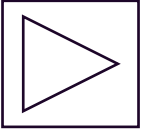


The Circuit

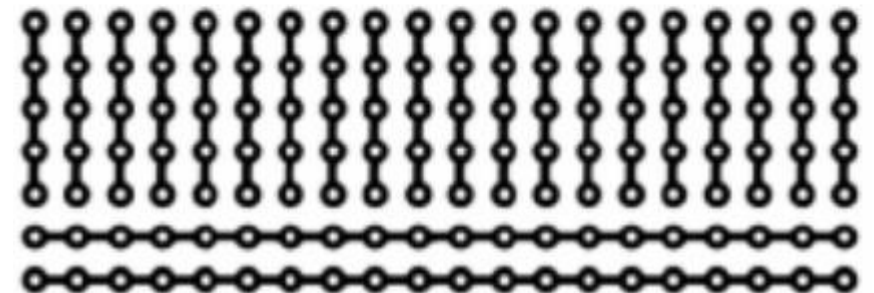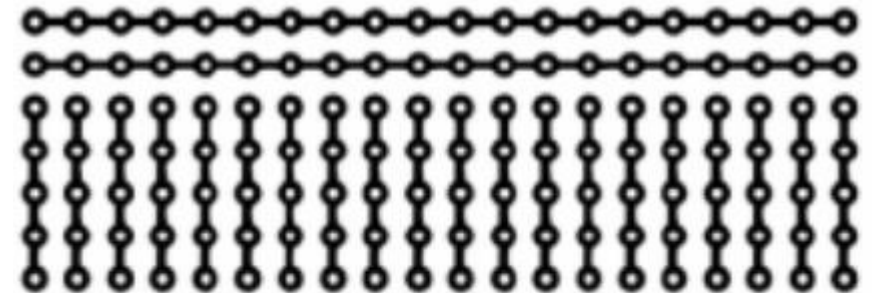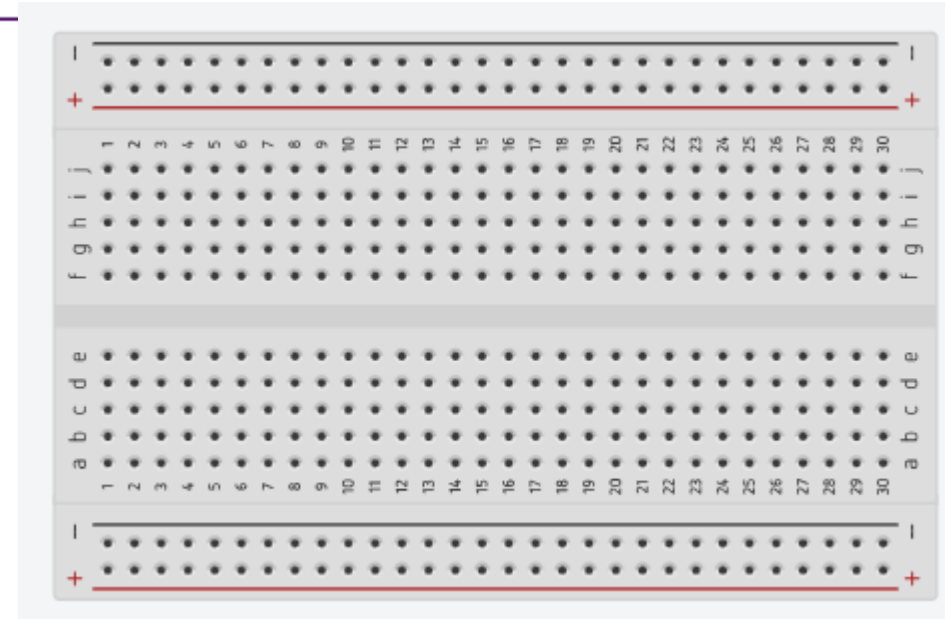- It is a reusable board used to build electronic circuit prototypes without the need for soldering. Also called protoboard, it is made of perforated plastic blocks and several thin strips of copper metal alloy.




Multiple LEDs

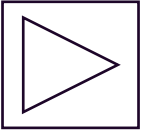

The Code


```
set animationSpeed to 400
set built-in LED to HIGH
wait animationSpeed milliseconds
set built-in LED to LOW
wait animationSpeed milliseconds
set pin 12 to HIGH
wait animationSpeed milliseconds
set pin 12 to LOW
wait animationSpeed milliseconds
set pin 11 to HIGH
```
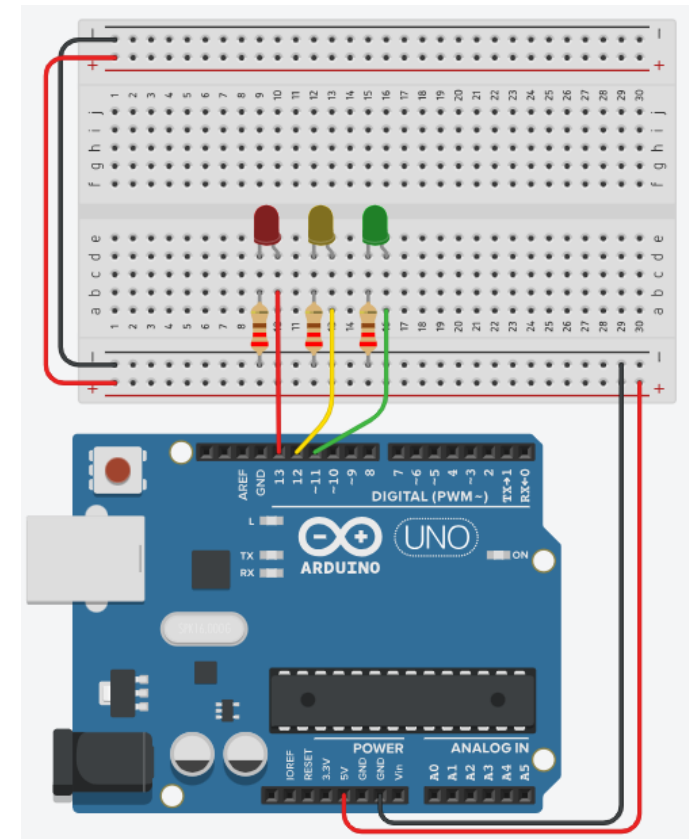
```
wait animationSpeed milliseconds
set pin 11 to LOW
wait animationSpeed milliseconds
```



Introduction to variables

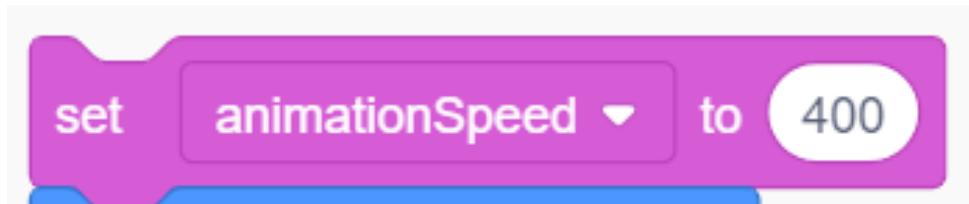
- Variables are placeholders in memory, so they are widely used to store data that needs to be used later.
- Variables need to be declared before being used, and for that, it is necessary to assign a specific type, allowing to reserve in memory the necessary space for the information that will be stored.



≡

```
int animationSpeed = 0;  
animationSpeed = 400;
```

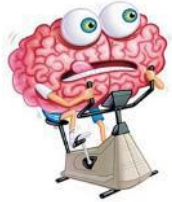- Integer (int) is a variable type that will hold a numeric (integer) value.



Practice Questions


1. Create a Two-Way Traffic Light System. For this project, you need to create two different traffic lights (using three LEDs for each), and they should work as follows:

Traffic Light System 1:

1. Red LED ON;
2. Red LED ON;
3. Red LED ON;
4. Red LED ON;
5. Red LED ON for 0.5 seconds;
6. Yellow LED ON for 1 second;
7. Green LED ON for 4 seconds;
8. Yellow LED ON for 1 second;
9. Repeat.

Traffic Light System 2:

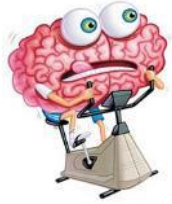1. Red LED ON for 0.5 seconds;
2. Yellow LED ON for 1 second;
3. Green LED ON for 4 seconds;
4. Yellow LED ON for 1 second;
5. Red LED ON;
6. Red LED ON;
7. Red LED ON;
8. Red LED ON;
9. Repeat.



Practice Questions

1. A set of 4 LEDs connected to pins 2 to 5 will be activated sequentially when powering the Arduino. The LEDs will turn off after 2 seconds. And the process restarted 0.5 seconds later. Create variables to define and hold the waiting time value.
2. Make a sequence of six LEDs light up as follows: those present at BOTH ends of the sequence should already be ON when powering the Arduino. Then, sequentially turn the lights ON, one towards the other, giving the impression that they are meeting. Then, return to the ends giving the impression that they are moving away.

Digital Inputs – Push Button

- The button is a component that connects two circuit points when pressed. In this example, the LED is ON while the button is pressed.


i What will I learn?

- Read a digital input.
- Use If conditionals.
- Use pushbuttons.
- Pull Up setting.


i Components



Pushbutton

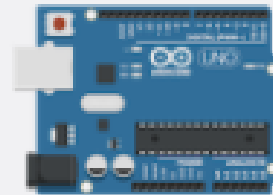

Arduino Uno
R3

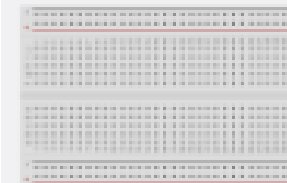

Breadboard
Small




Resistor




LED

Digital Inputs – Push Button

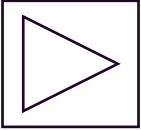


The Circuit

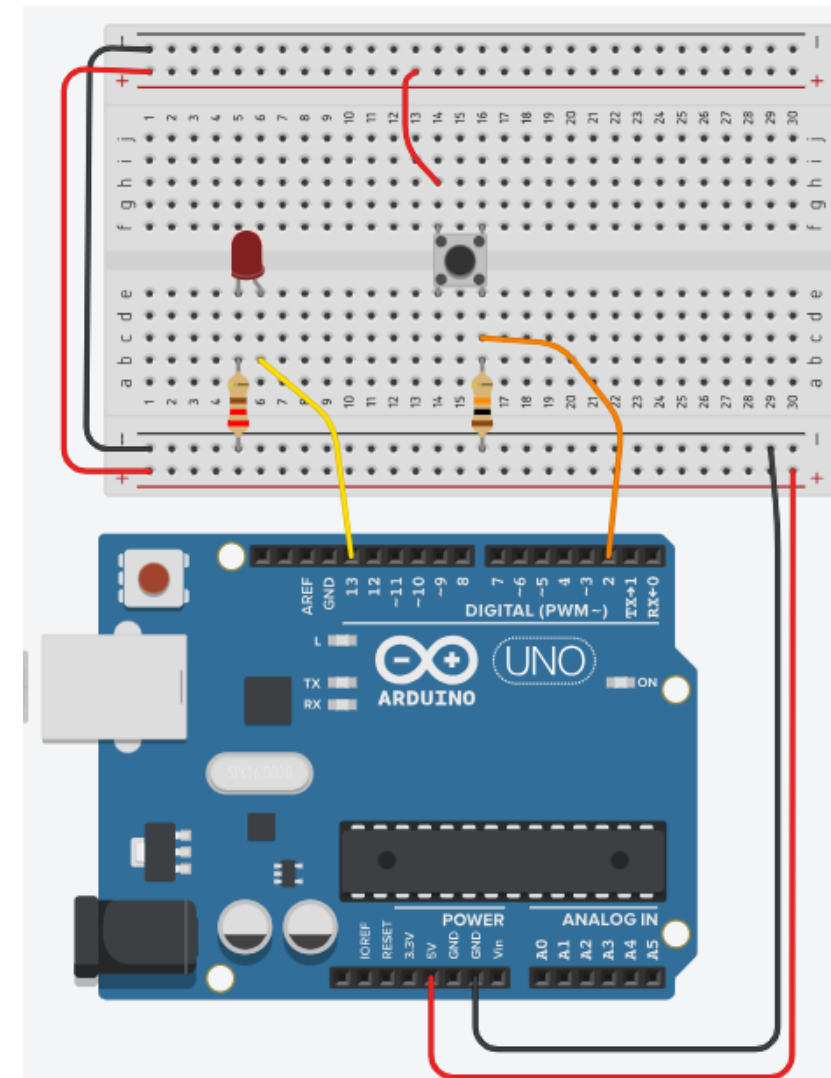- You will need:
 - 1 Arduino Uno board.
 - 1 LED.
 - 2 Resistors (220 Ω and 10k Ω).
 - 1 Breadboard.
- Connect all components like in the following image:




Pull Up and Pull Down

- Normally, when you connect pushbuttons to digital pins on a microcontroller, the pin switches to a floating-point state when the pushbutton is open.
- Floating point: a state is assumed at random. In the case of Arduino, it normally assumes the high level (bit 1).
- Resistors are employed in order to avoid the floating point, fixing a voltage value applied under a pin even when the button is open. When a resistor is connected to the power source (setting the pin high), it is called Pull Up. If it is connected to the ground (setting the pin at a low level), it is called Pull Down.

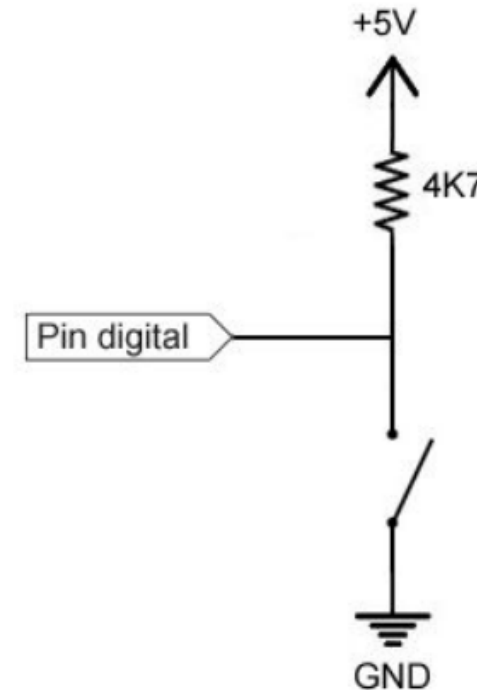


Pull Up

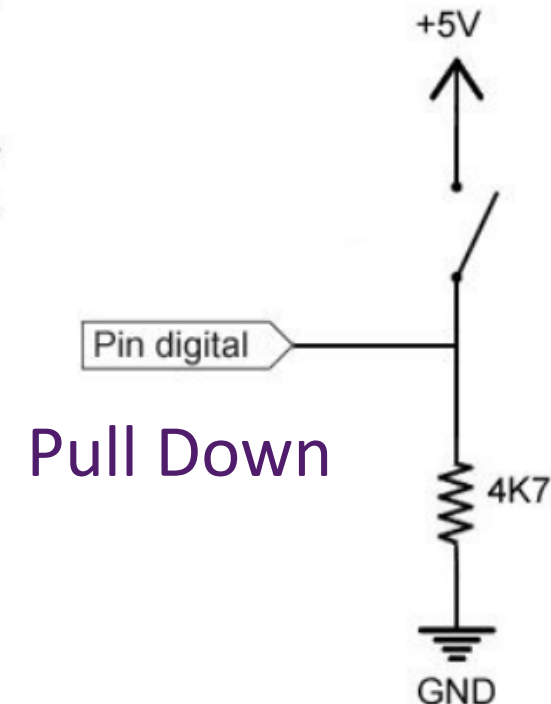Pull Up resistors should have high values, e.g., above 10k Ω .




Pull Down

Digital Inputs – Push Button

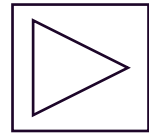

The Code

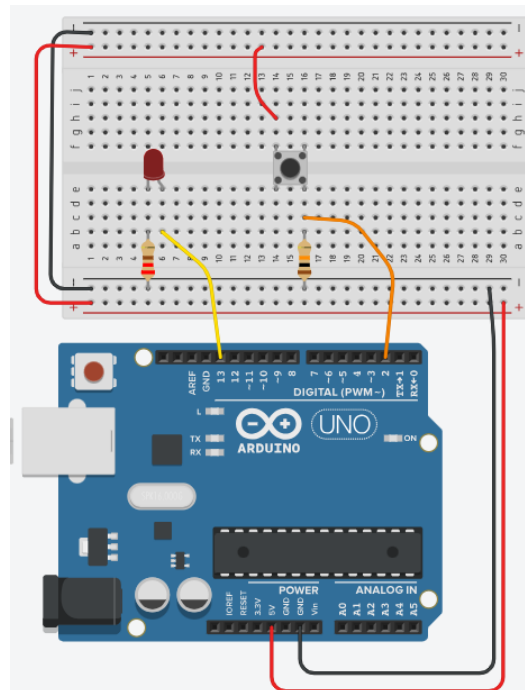- if conditional: enables to execute different commands based on a condition.
- set variable (Pink): modify the value of a variable.
- read digital pin Input Command (Purple): read the value the pin receives.



```

comment read the state of the pushbutton
set buttonState to read digital pin 2
comment check if pushbutton is pressed. if it is, the ...
if buttonState = HIGH then
  set built-in LED to HIGH
else
  set built-in LED to LOW
  
```

If conditional

- The if conditional is used to test whether a given condition is true. For example, check whether an input pin's value is above a certain number. It is usually used in conjunction with operators.

```
if (x > 120){  
    digitalWrite(LEDpin1, HIGH);  
    digitalWrite(LEDpin2, HIGH);  
}
```

Operator

Conditional


If – else conditional

- When the if condition is false, the else is executed instead. We can also define multiple conditions using the else if.

```
if (pinFiveInput < 500)
{
  // do Thing A
}
else if (pinFiveInput >= 1000)
{
  // do Thing B
}
else
{
  // do Thing C
}
```

Conditional

Operator

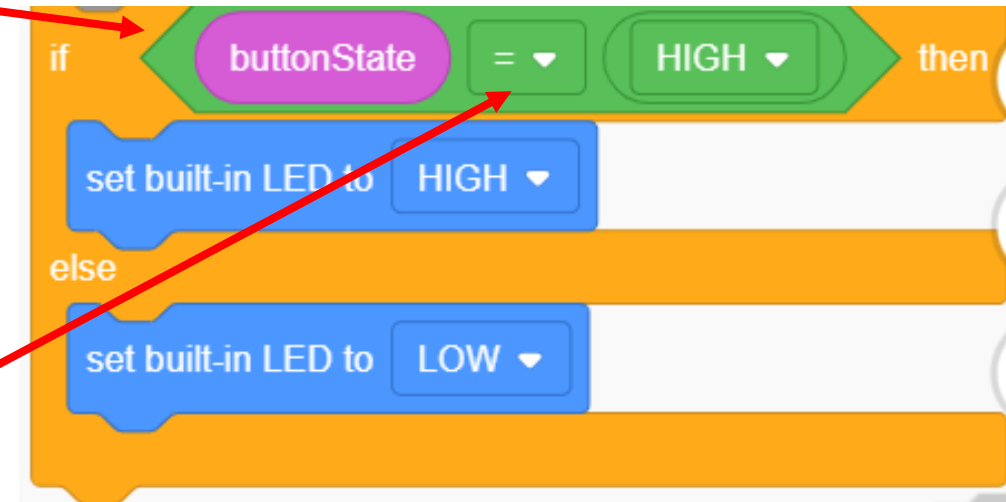

Comparison and Arithmetic Operators

- Operators are useful not only to perform operations but to build conditionals.

✓	<	Less than
	<=	Less than or equal to
	=	Equal to
	≠	Not equal to
	>	Less than
	>=	Less than or equal to

Comparison operators

✓	+	Addition
	-	Subtraction
	×	Multiplication
	/	Division
	%	Modulus
	^	Power

Arithmetic operators

```

if (buttonState == HIGH) then
  set built-in LED to HIGH
else
  set built-in LED to LOW
  
```



Practice Questions

1. Button and LED: When pressing a button connected to pin 8, an LED connected to pin 10 should turn ON in such a way that it should remain ON for 5 seconds, and after that time, the LED will turn OFF.
2. LED Bar: A set of 4 LEDs connected to pins 2 to 5 will be activated sequentially after button 1 (connected to pin 10) is pressed.
3. LED Bar: A set of 4 LEDs will activate sequentially after button 1 is pressed. The LEDs will be deactivated by a button 2.
4. Create a circuit with one LED and two buttons. The LED should be connected to pin 13, and the buttons to any digital pin you choose. Your system should turn ON the LED when pressing buttons 1 or 2.
5. Create a circuit with two LEDs and two buttons. Each LED should be turned ON by one of the buttons.


Analogue Inputs

- In this example, you will learn how to read an analogue input. The value read from the input will be used to control the blinking time of the onboard LED using a potentiometer. The potentiometer is a resistor with a varying resistance.


i What will I learn?

- Read an analogue input.
- Use a potentiometer.

i Components

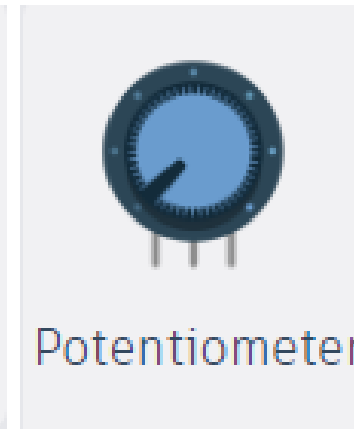


Analogue Inputs

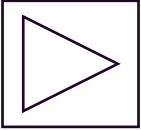

The Circuit

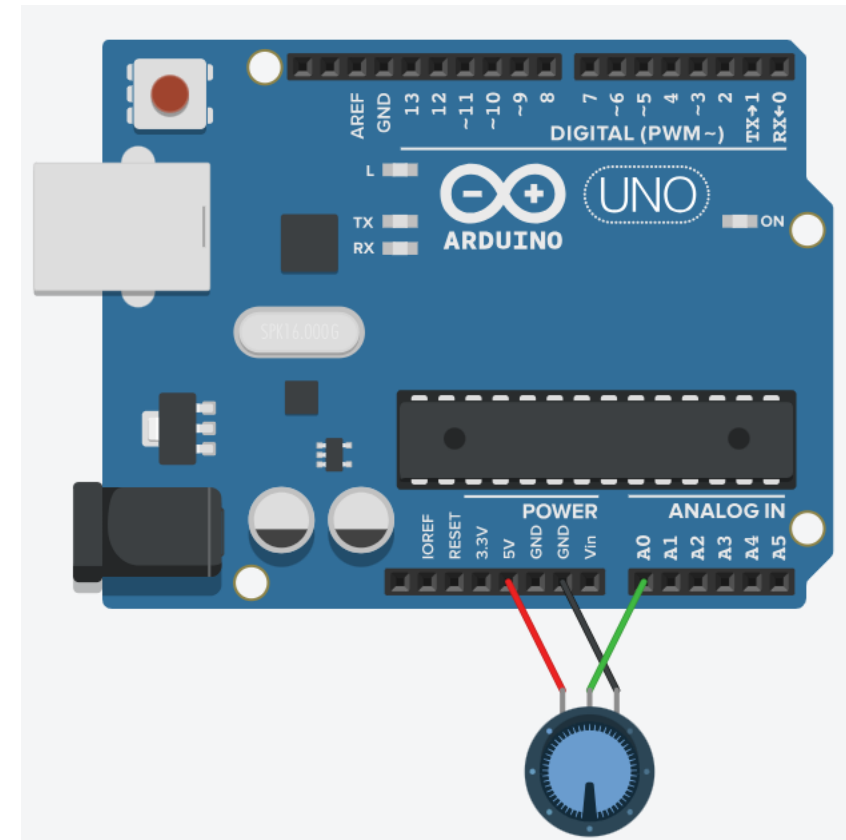- A potentiometer is a resistor whose value is variable, suitable for use as a control element in electronic devices. The resistance between the centre and end terminals varies according to the position of the centre control switch.
- Note that the end terminals are connected to the source (5V) and ground (GND), while the central terminal is connected to an Arduino analogue pin.



Analogue Inputs

The Code

- Initially, the analogue pin is read, and its value is stored in the variable “sensorValue.”
- The onboard LED (pin 13) turns ON.
- Pause the code for “sensorValue” milliseconds. This pause allows us to continue seeing the LED ON.
- The onboard LED (pin 13) turns OFF.
- Pause the code for “sensorValue” milliseconds. This pause allows us to continue seeing the LED OFF.
- Repeat.

```
forever
  comment read the value from the sensor
  set sensorValue to read analog pin A0
  comment turn the LED on
  set built-in LED to HIGH
  comment stop the program for the <sensorValue> millise...
  wait sensorValue milliseconds
  comment turn the LED off
  set built-in LED to LOW
  comment stop the program for the <sensorValue> millise...
  wait sensorValue milliseconds
```

The image shows a Scratch code block for a 'forever' loop. The code consists of the following blocks in order: a comment block 'read the value from the sensor', a 'set' block for 'sensorValue' to 'read analog pin A0', a comment block 'turn the LED on', a 'set built-in LED to' block set to 'HIGH', a comment block 'stop the program for the <sensorValue> millise...', a 'wait' block for 'sensorValue' milliseconds, a comment block 'turn the LED off', a 'set built-in LED to' block set to 'LOW', a comment block 'stop the program for the <sensorValue> millise...', and a final 'wait' block for 'sensorValue' milliseconds.

Analogue to Digital Converter (ADC)

- The Arduino UNO has 1 ADC to convert the signals inserted in pins A0 to A5. This ADC has a 10-bit resolution and accepts voltages ranging from 0V to 5V (it does not accept negative values).
- The voltage values read will be converted into a range from 0 to 1023, as $2^{10} = 1024$. Thus:

$$5V - 1023$$


Serial Monitor

- In this example, you will learn how to display data using the serial monitor. As the name suggests, the serial monitors the data transferred between the Arduino and the computer.

i What will I learn?

- Use the serial monitor.

i Components

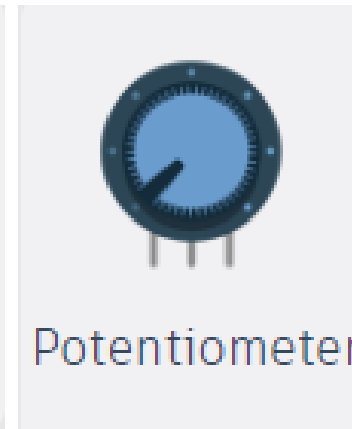


Serial Monitor



- To access the serial monitor, click on Code and Serial Monitor.
- You can use the Send and Clear buttons to send information and delete all data shown on the monitor.
- The graph button shows the values in the form of a graph.

The screenshot displays the Arduino IDE interface. The 'Code' button in the top right corner is highlighted with a red box. The 'Serial Monitor' button in the bottom right corner is also highlighted with a red box. The main workspace shows a block-based code editor with several blocks: 'set built-in LED to HIGH', 'set pin 0 to HIGH', 'set pin 3 to 0', 'rotate servo on pin 0 to 0 degrees', 'play speaker on pin 0 with tone 60', and 'turn off speaker on pin 0'. A 'forever' loop block contains a 'comment' block, a 'set sensorValue to read analog', another 'comment' block, and a 'print to serial monitor sensorValue' block. The Serial Monitor window at the bottom is empty, with 'Send', 'Clear', and 'Graph' buttons highlighted with a red box.

Serial Monitor

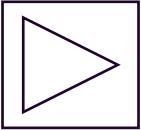


The Circuit

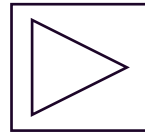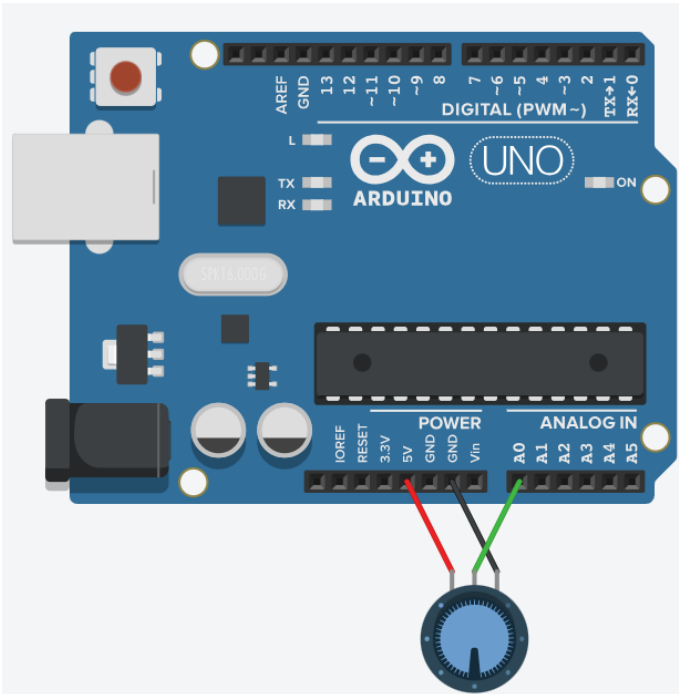


The Code

```

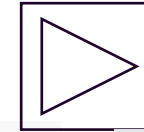forever
  comment read the input on analog pin 0:
  set sensorValue to read analog pin A0
  comment print out the value you read:
  print to serial monitor sensorValue with newline
  
```




The Monitor

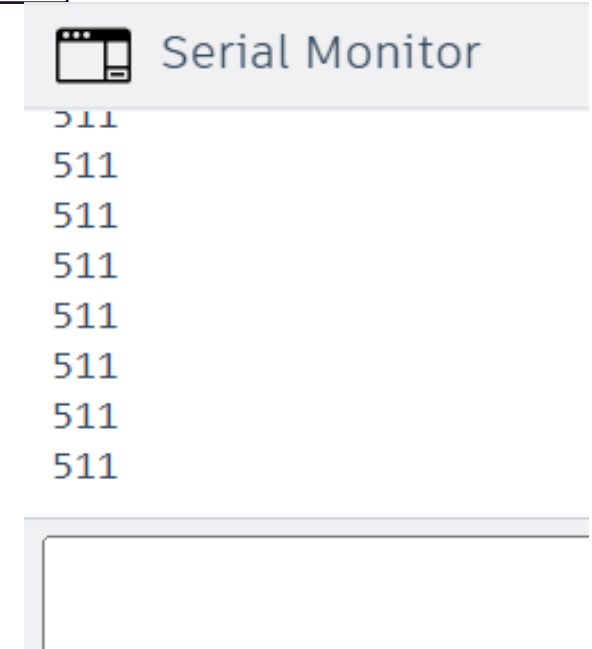


- print to serial monitor Output command (blue): enables sending data to the serial monitor. The newline option skips to the next line after printing the data.



Serial Monitor

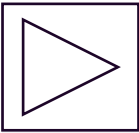

The Circuit

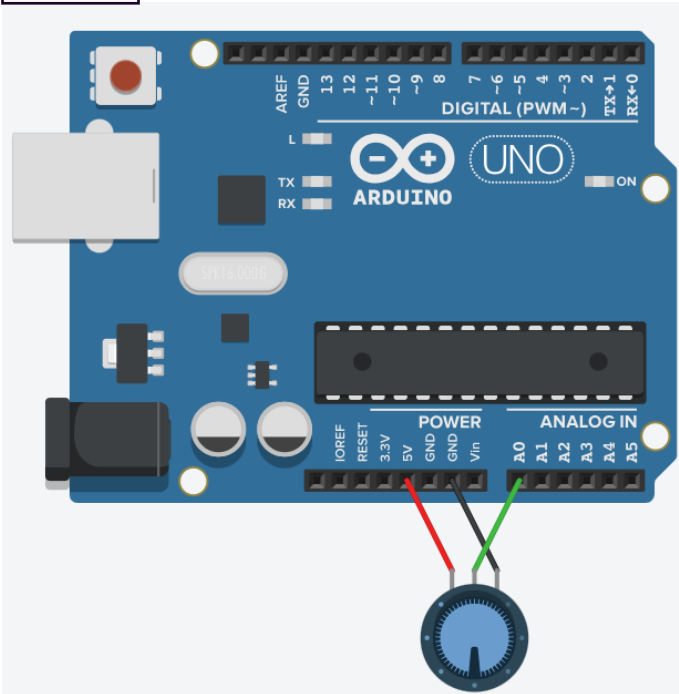

The Code

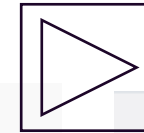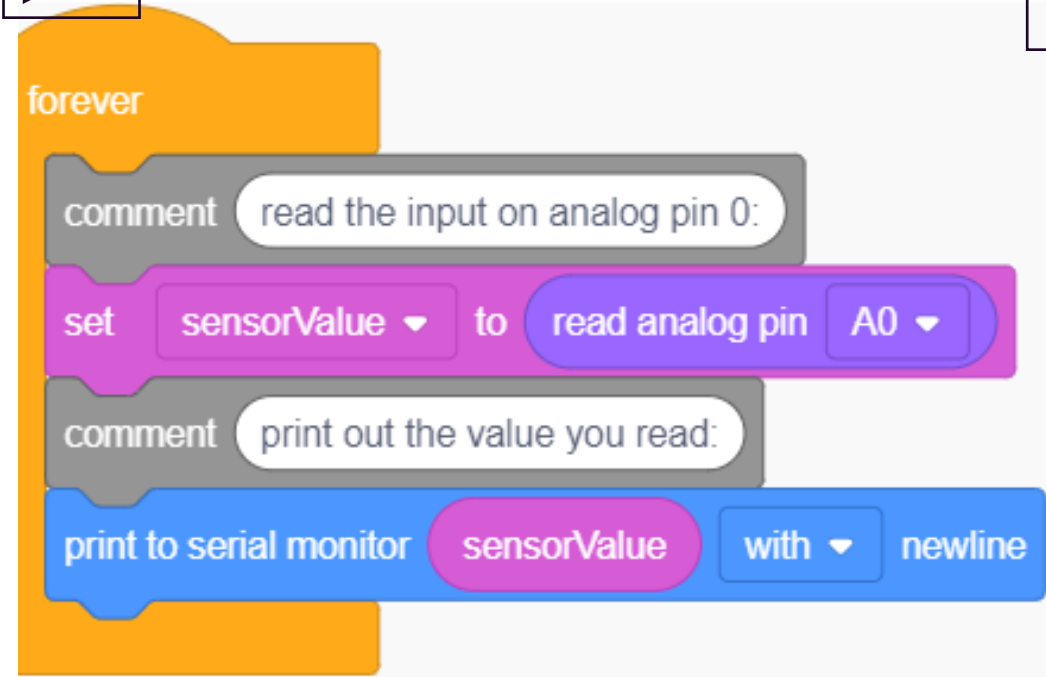

The Monitor



Serial Monitor

```

511
511
511
511
511
511
511
511
511
511
  
```

- As you rotate the central terminal of the potentiometer towards 5V, the value approaches 1023. Meanwhile, as you rotate it towards the GND, the value approaches 0.

Analogue Outputs

- In this example, you will learn how to write an analogue output. For the Arduino Uno, an analogue output means using a Pulse Width Modulation (PWM). For this purpose, only digital pins with the tilde symbol can be used.


i What will I learn?

- Write an analogue output.
- Learn the count code block.

i Components




Analogue Outputs

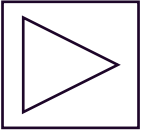

The Circuit

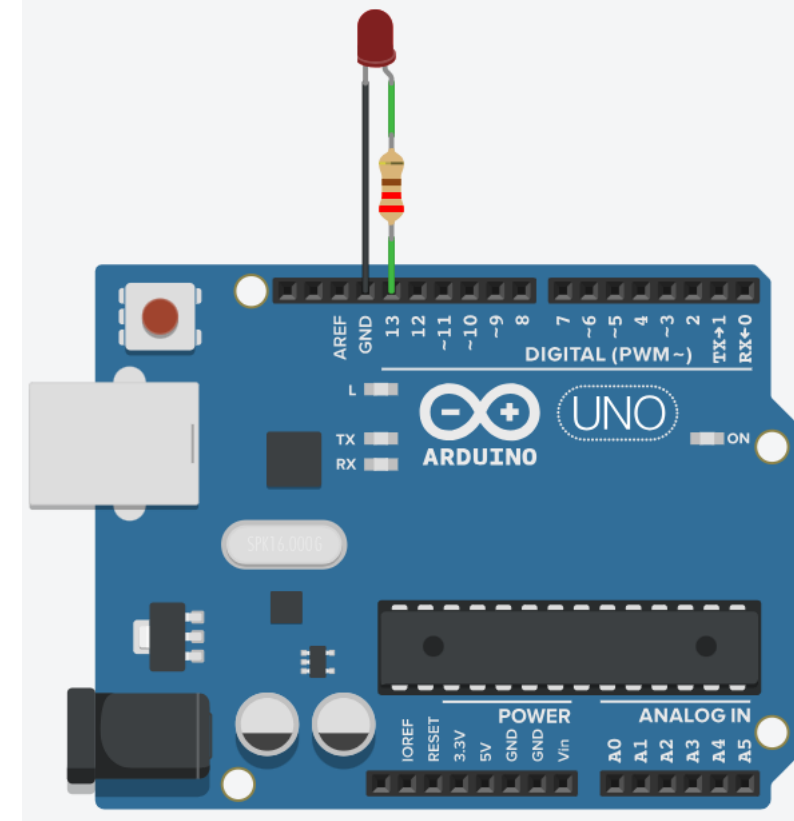
- This is the same circuit we have seen for the Hello World with an External LED example.



Analogue Outputs

The Code

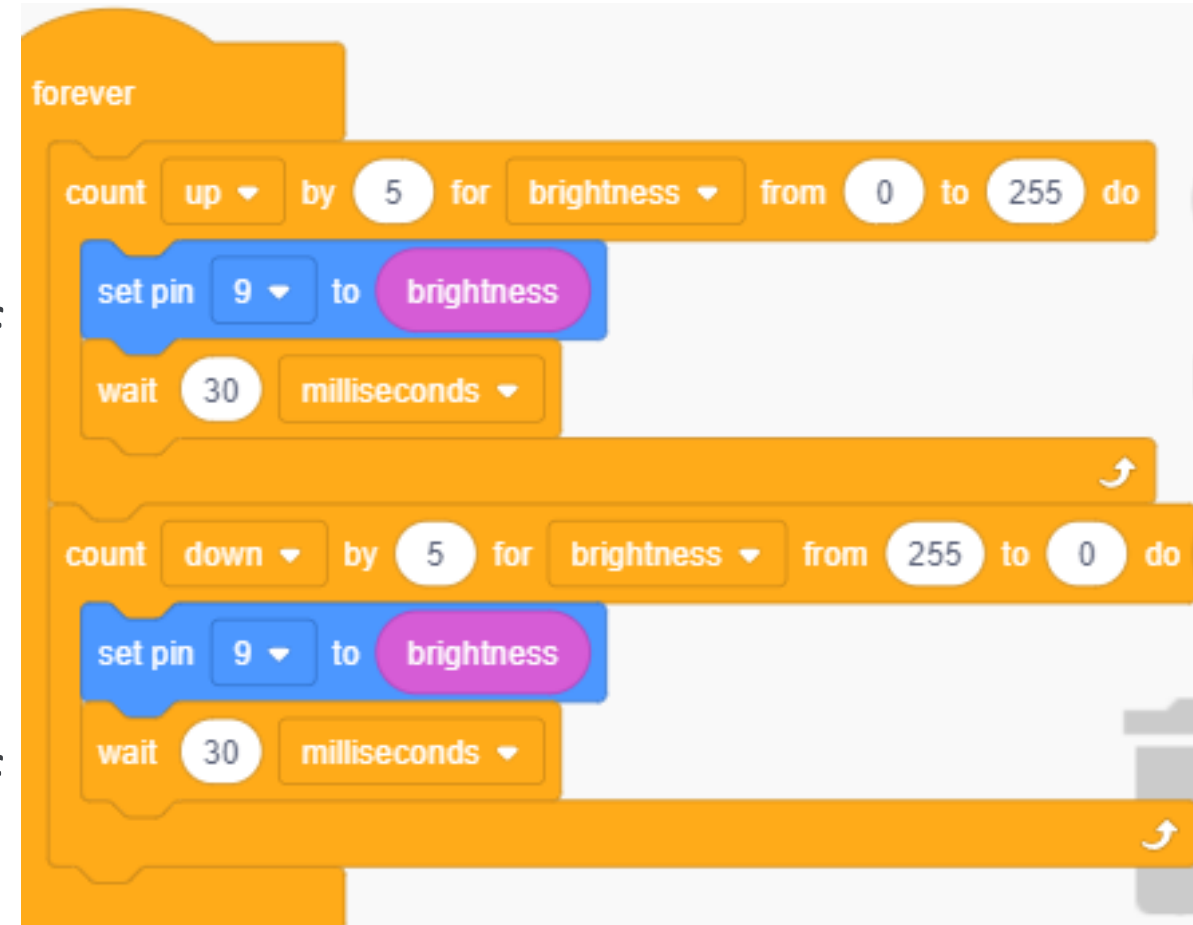- count control command (yellow): counts (up or down) the changing step of a variable value. In addition, it implements a for loop that defines the range of values the variable value can assume.
- This creates a PWM. A PWM changes the voltage applied to a load allowing us to control its parameters. For example, if the load is an LED, we can control its brightness.



```
forever
  count up by 5 for brightness from 0 to 255 do
    set pin 9 to brightness
    wait 30 milliseconds
  count down by 5 for brightness from 255 to 0 do
    set pin 9 to brightness
    wait 30 milliseconds
```

The image shows a Scratch script for generating a PWM signal. It starts with a 'forever' loop. Inside the loop, there are two 'count' blocks. The first 'count' block is set to 'up' by 5 for 'brightness' from 0 to 255. This is followed by a 'set pin 9 to brightness' block and a 'wait 30 milliseconds' block. The second 'count' block is set to 'down' by 5 for 'brightness' from 255 to 0. This is also followed by a 'set pin 9 to brightness' block and a 'wait 30 milliseconds' block. The script is designed to create a square wave pulse that varies in width, effectively creating a PWM signal.

Summary

We introduced the Arduino Platform and Microcontrollers. ✓

We simulated prototypes to practice digital and analogue input/outputs. ✓

We learned the electronic components: LED, resistor, potentiometer, breadboard, and pushbutton. ✓

We learned programming: creating variables, if conditionals, for loops, reading and writing to digital pins. ✓

We learned how to send data to the serial monitor ✓

4. Arduino: Sensors and Actuators


Light-Dependent Resistor (LDR)

- In this example, you will learn how to read the LDR sensor. LDR is a photoresistor whose resistance value varies according to the incident light. It has a low resistance value in the presence of light and a high value in its absence.

What will I learn?

- Write an analogue output.
- Use and LDR.

Components

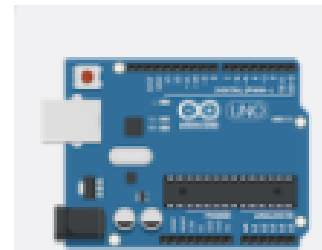

Arduino Uno
R3



Photoresistor




Resistor




LED

LDR Sensor

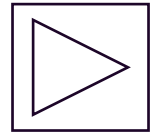


The Circuit

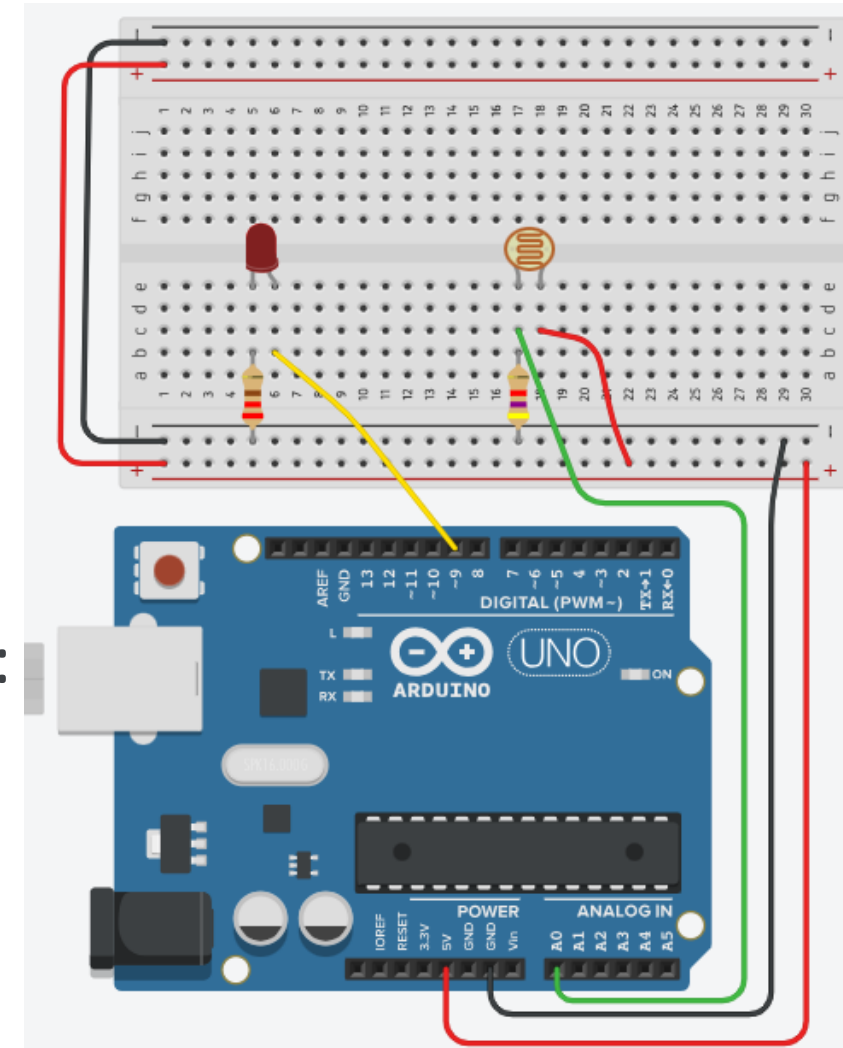- You will need:
 - 1 Arduino Uno board.
 - 1 LED.
 - 2 Resistors (220 Ω for the LED and 4.7k Ω for the LDR).
 - 1 Breadboard.
-
- Connect all components like in the following image:




LDR Sensor

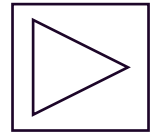


The Circuit

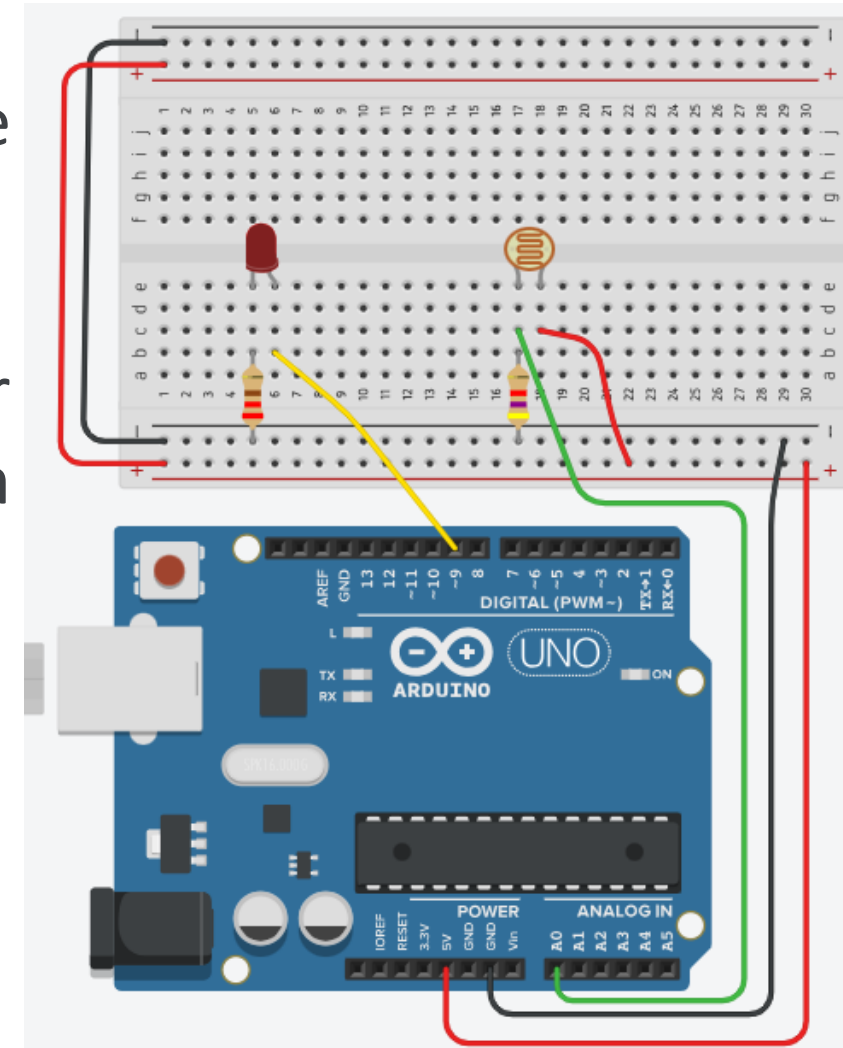- Note that the LDR has two terminals and can be connected in any way, like any other resistor.
- The LDR must be connected in series with another resistor and connect the Arduino pin in between them.



LDR Sensor

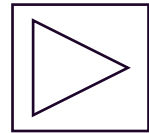

The Code

- The map function converts any value to a desirable range.
- In this example, we are converting 'sensorValue' in the range 0 to 255, as follows:

$$\frac{\textit{sensorValue}}{255}$$

```

comment read the value from the sensor
set sensorValue to read analog pin A0
comment print the sensor reading so you know its range
print to serial monitor sensorValue with newline
comment map the sensor reading to a range for the LED
set pin 9 to map sensorValue to range 0 to 255
wait .1 secs
  
```


Ultrasonic Sensor

- In this example, you will learn how to read the Ultrasonic sensor. It allows measuring distances based on sound signals.


i What will I learn?

- Use an Ultrasonic sensor.

i Components

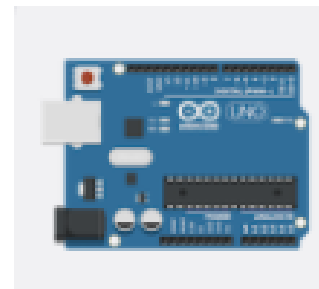


Arduino Uno
R3

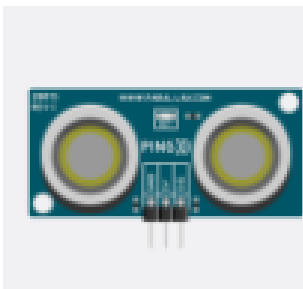

Ultrasonic
Distance...

Ultrasonic Sensor

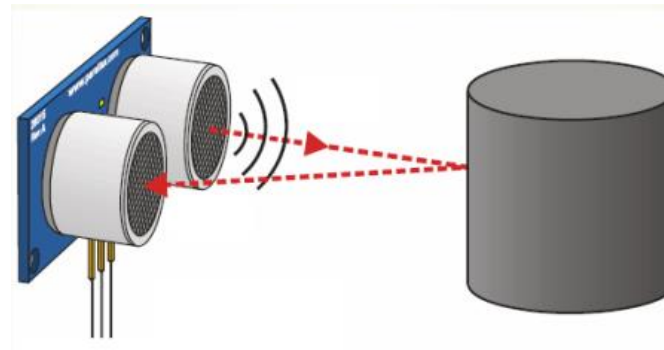- The ultrasonic distance sensor consists of a transmitter and receiver capable of measuring distances based on the speed of sound in the air.




- When given a pulse on the trigger pin, the transmitter emits a sound signal. When hitting an object, this sound signal is reflected to the sensor, where the receiver captures it (echo pin). The time taken from the transmission of the sound signal to its capture by the receiver can be used to determine the object's distance based on the sound propagation speed in the air (340m/s).

Ultrasonic Sensor


The Circuit

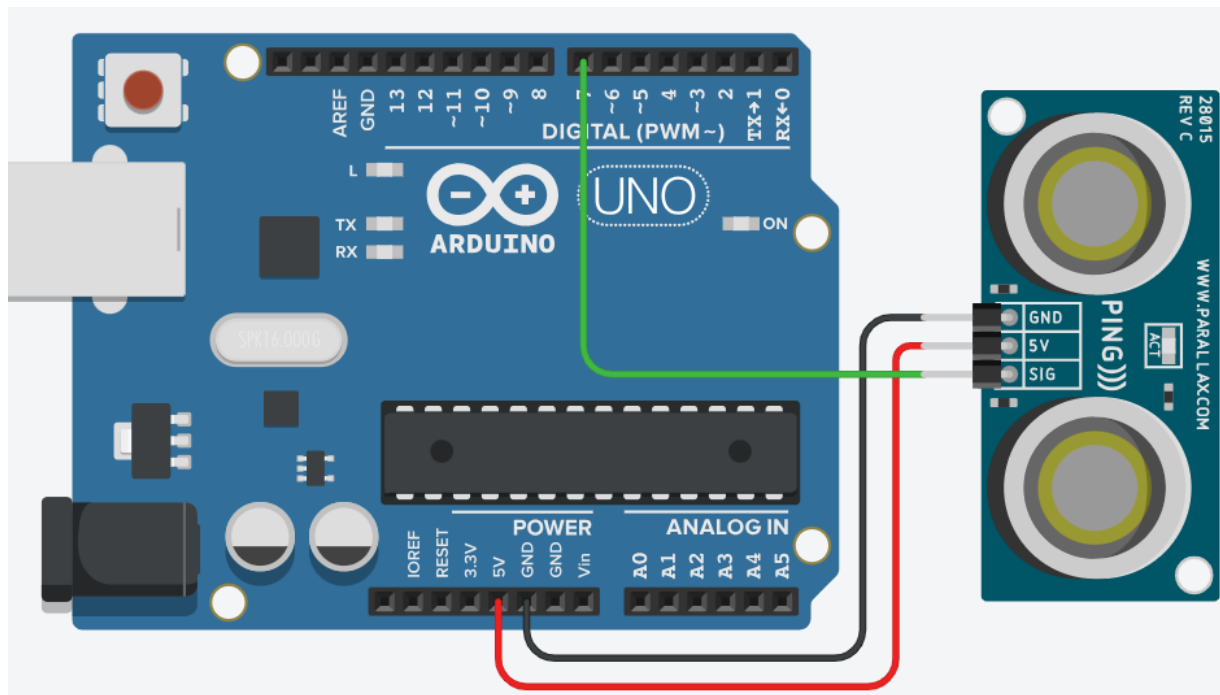- In this example, the transmitter and receiver are represented by the signal (SIG) pin, which is connected to pin 7.



- Note the need to connect to the 5V and GND.

Ultrasonic Sensor

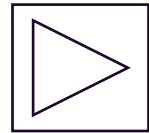

The Code

- The read ultrasonic input command reads the object's distance in cm.
- The value in cm is then converted to inches and stored in the variable *inches*.

```

forever
  comment measure the ping time in cm
  set cm to read ultrasonic distance sensor on trigger pin 7 echo pin same as trigger in units cm
  comment convert to inches by dividing by 2.54
  set inches to cm / 2.54
  print to serial monitor inches without newline
  print to serial monitor in, without newline
  print to serial monitor cm without newline
  print to serial monitor cm with newline
  wait .1 secs
  
```



Practice Questions

1. Use an Ultrasound sensor to light up 2 LEDs according to the distance between an object and the sensor. If the object is close, a red LED should turn ON; otherwise, a green LED should turn ON.
2. Repeat the previous question and replace the red LED with a buzzer (search on Tinkercad for Piezo).
3. Now, use an LDR sensor to light up 2 LEDs according to the light's intensity. If the intensity is low, a red LED should turn ON; otherwise, a green LED should turn ON.

Summary

We introduced the Arduino Platform and Microcontrollers. ✓

We simulated prototypes to practice digital and analogue input/outputs. ✓

We learned the electronic components: LED, resistor, potentiometer, breadboard, and pushbutton. ✓

We learned the programming: creating variables, if conditionals, reading and writing to digital pins. ✓

We learned how to send data to the serial monitor ✓

Thank you!

Leonardo.Alves-Dias@warwick.ac.uk